



The Configurable System-on-Chip Company

**The Triscend E5
Configurable System
Interconnect (CSI) Bus**


July 1999

Agenda

- The Basics
- Address Selectors
- Converting an Existing 8032 Design
- Creating Address Structures
- DMA Operations
- The CSI Bus Simulation Model
- Wait-State and Breakpoint
- Summary and Questions

Bus Basics

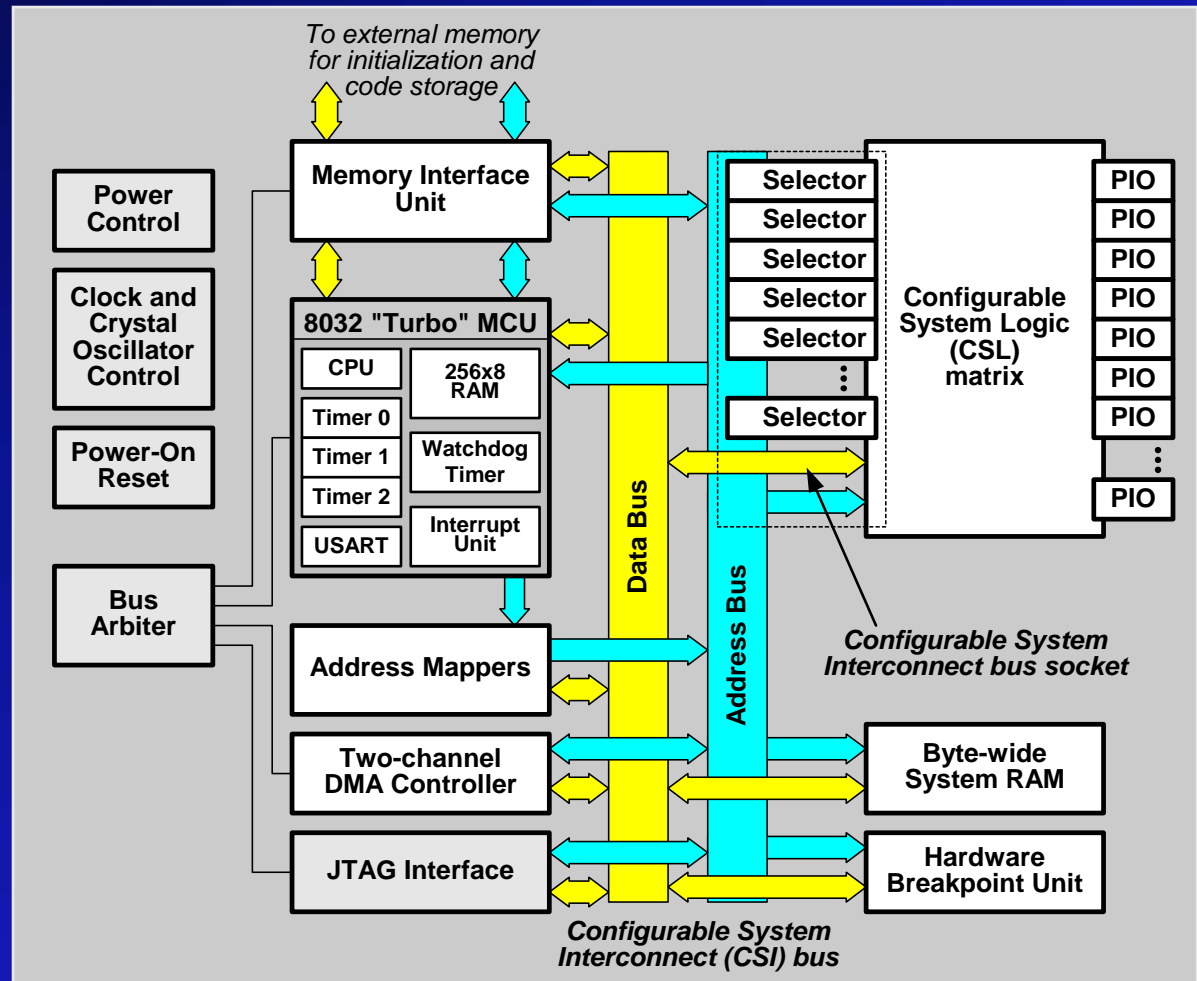- Bus Master
 - 8032
 - DMA
 - JTAG
- Arbiter
- Bus Slave




Language Basics

- **VHDL** (VHSIC Hardware Description Language)
 - Widely used for logic synthesis and simulation
 - CSI Bus primitives cannot be inferred, must be instantiated
 - CSI Bus can be simulated using VHDL
- **Verilog** (no examples here)
- **Chisel** ('C'-like Hardware Specification Language)
 - Triscend proprietary language
 - Not intended for customer use


CSI Bus Basics

What is the CSI Bus?

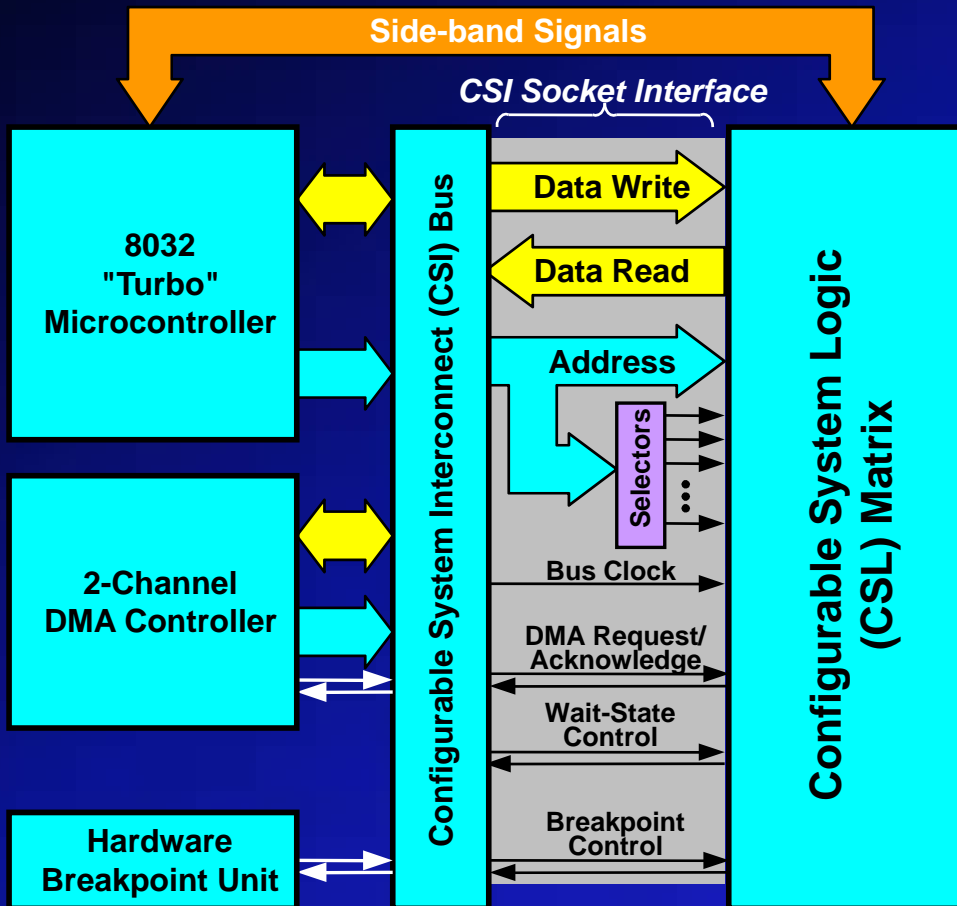


- Distributes address, data, and control to functions in the CSL Matrix
- Predictable timing
- Future compatible

Example: Read/Write Register

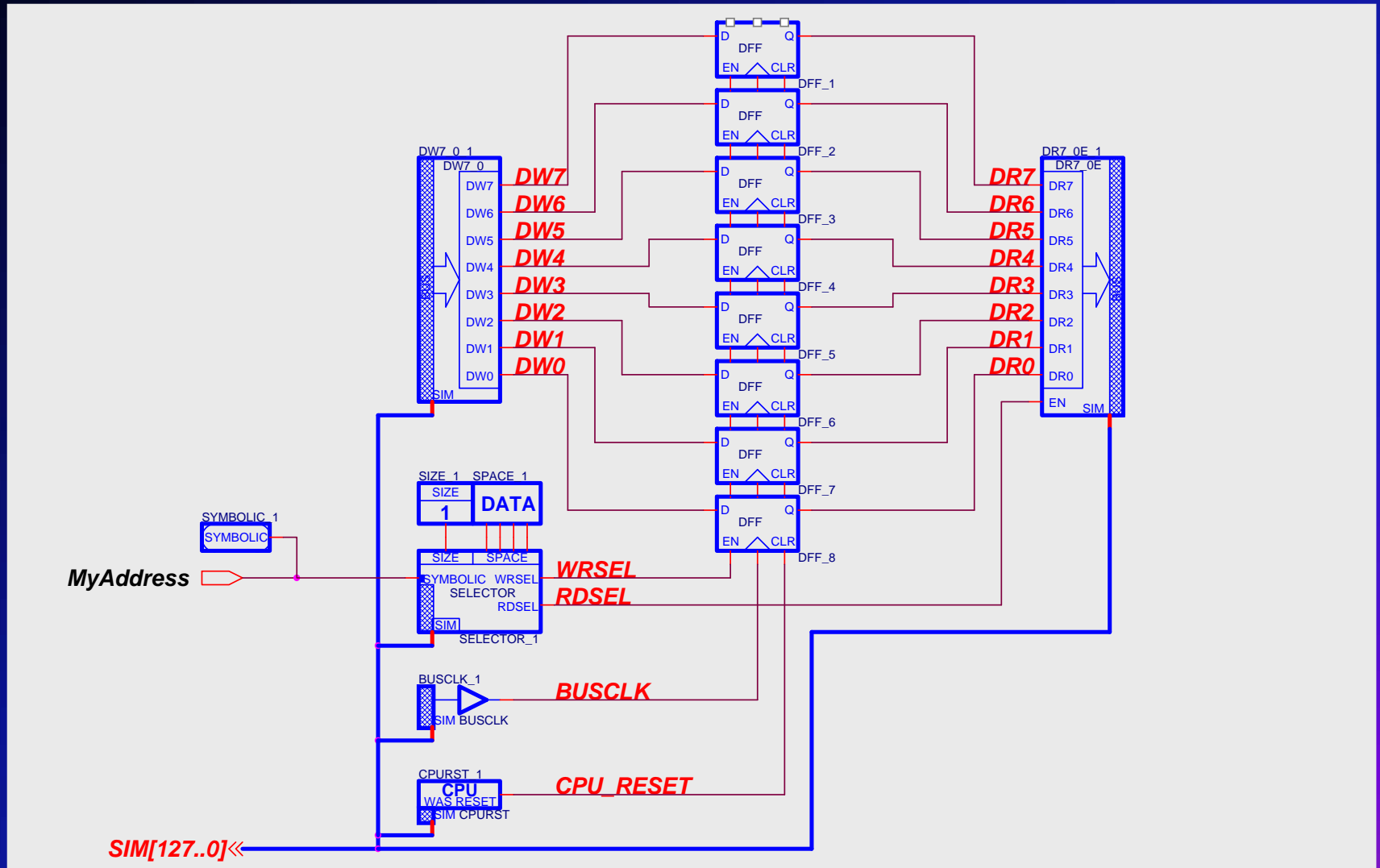

Data Write

Schematic

 

- Data provided by bus master
- Data available on every BusClock edge (assuming no wait-states)

Data Write (VHDL)

Instantiate

architecture TRISCEND of MYDESIGN is

component DW7_0

port (

DW7 : out std_logic;

DW6 : out std_logic;

DW5 : out std_logic;

DW4 : out std_logic;

DW3 : out std_logic;

DW2 : out std_logic;

DW1 : out std_logic;

DW0 : out std_logic;

SIM : inout std_logic_vector(127 downto 0)

);

end component;

Use

begin

MYDW7 : DW7_0 port map (

DW7 => my_dw_bus(7),

DW6 => my_dw_bus(6),

DW5 => my_dw_bus(5),

DW4 => my_dw_bus(4),

DW3 => my_dw_bus(3),

DW2 => my_dw_bus(2),

DW1 => my_dw_bus(1),

DW0 => my_dw_bus(0)


);

Data Write (Chisel)

```
module example {  
  
    parameter int component_width = 8;  
  
    output [component_width] dw;  
  
    for (int i=0; i < component_width; i++) {  
        datain str("DW_",i) (.o=dw[i], :bit=i);  
    }  
  
}
```


Data Read

Schematic

 

- Data provided by currently addressed slave
- Assert EN to enable data onto the CSI bus
- Data Read is a contention-free wired-OR bus

CSI Data Flow

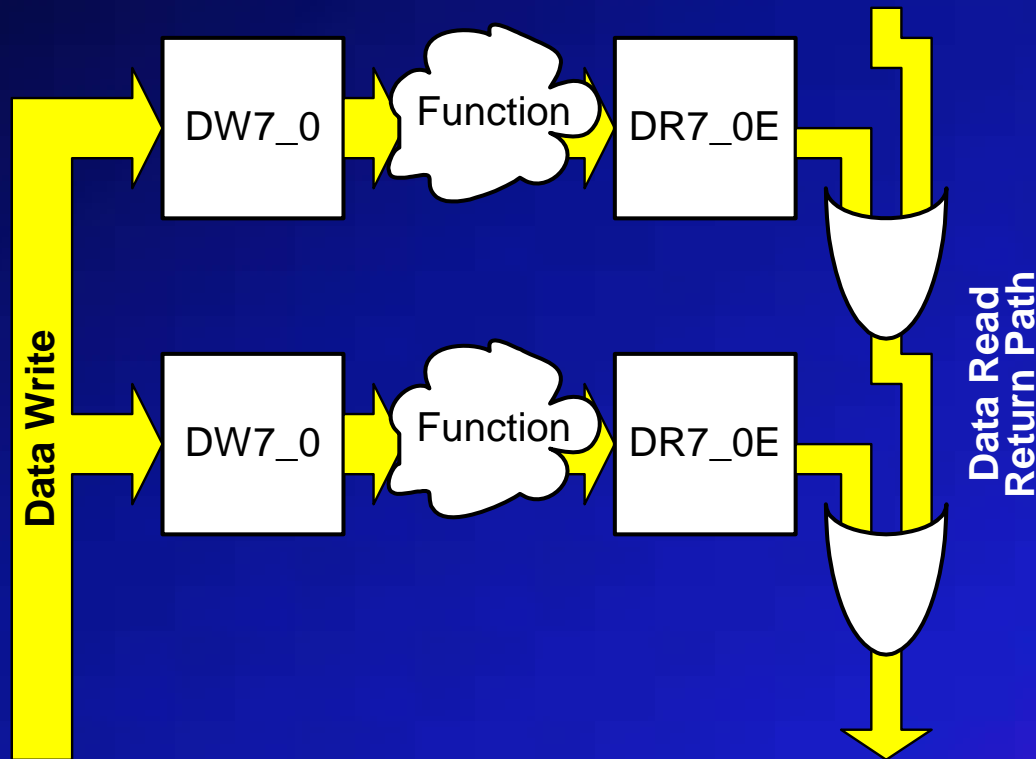

- Return path is OR-ed
- Contention-free, not conflict-free

Data Read (VHDL)

Instantiate

architecture TRISCEND of MYDESIGN is

component DR7_0E

port (

DR7 : in std_logic;

DR6 : in std_logic;

DR5 : in std_logic;

DR4 : in std_logic;

DR3 : in std_logic;

DR2 : in std_logic;

DR1 : in std_logic;

DR0 : in std_logic;

EN : in std_logic;

SIM : inout std_logic_vector(127 downto 0)

);

end component;

Use

begin

MYDR7_0E : DR7_0E port map (

DR7 => my_dr_bus(7),

DR6 => my_dr_bus(6),

DR5 => my_dr_bus(5),

DR4 => my_dr_bus(4),

DR3 => my_dr_bus(3),

DR2 => my_dr_bus(2),

DR1 => my_dr_bus(1),

DR0 => my_dr_bus(0),

EN => my_read_select


);

Data Read (Chisel)

```
module example {  
  
    parameter int component_width = 8;  
  
    input [component_width] dr;  
    net [component_width] dr_dmux;  
    input rdssel;  
  
    for (int i=0; i < component_width; i++) {  
        dmux str("DR_DMUX_",i) (.d=dr[i], .s=rdssel, .o=dr_dmux);  
    }  
    for (int i=0; i < component_width; i++) {  
        dataout str("DR_",i) (.i=dr_dmux[i], :bit=i);  
    }  
  
}
```

Address

Schematic

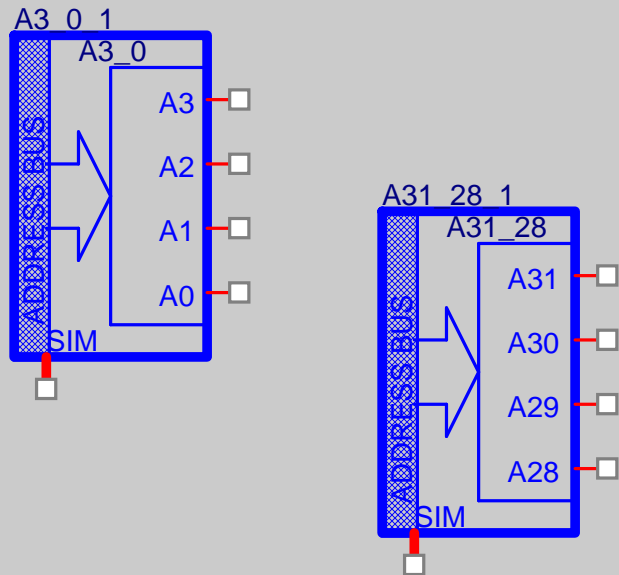

- Address provided by bus master
- Address available on every BusClock edge (assuming no wait-states)
- Up to 32-bits in 4-bit chunks

Address (VHDL)

Instantiate

architecture TRISCEND of MYDESIGN is

component A3_0

port (

A3 : out std_logic;

A2 : out std_logic;

A1 : out std_logic;

A0 : out std_logic;

SIM : inout std_logic_vector(127 downto 0)

);

end component;

Use

begin

MYA3_0 : A3_0 port map (

A3 => my_addr(3),

A2 => my_addr(2),

A1 => my_addr(1),

A0 => my_addr(0)

);

Available Components


- A31_28
- A27_24
- A23_20
- A19_16
- A15_12
- A11_8
- A7_4
- A3_0

Address (Chisel)

```
module example {  
    parameter int addr_width= 8;  
    output [addr_width] addr;  
    for (int i=0; i < addr_width; i++) {  
        addressin str("A_",i) (.o=addr[i], :bit=i);  
    }  
}
```

Bus Clock

Schematic

 

- Bus Clock drives the processor and all bus transactions
- Distributed globally within the device

Bus Clock (VHDL)

Instantiate

```
architecture TRISCEND of MYDESIGN is  
  
  component BUSCLK  
    port (  
      O      : out  std_logic;  
      SIM    : inout std_logic_vector(127 downto 0)  
    );  
  end component;
```

Use


```
begin  
  MYBUSCLK : BUSCLK port map (  
    O => my_local_clock  
  );
```

Bus Clock (Chisel)

```
module example {  
  
  output my_local_clock;  
  busclk (.o=my_local_clock);  
  
}
```

CPU Reset

Schematic

 

- Indicates that CPU was reset
 - Power-on
 - By application reset (RSTC)
 - By watchdog timer

CPU Reset (VHDL)

Instantiate

```
architecture TRISCEND of MYDESIGN is  
  
  component CPURST  
    port (  
      CPURST : out  std_logic;  
      SIM    : inout std_logic_vector(127 downto 0)  
    );  
  end component;
```

Use

```
begin  
  MYRST : CPURST port map (  
    CPURST => my_local_reset  
  );
```

CPU Reset (Chisel)

```
module example {  
    output my_reset;  
    cpurst (.cpurst=my_reset);  
}
```

Address Selectors

What is an Address?

- Three types of addresses for the E5
 - 8032 “**Logical**” address (16-bits, 64K)
 - E5 “**Physical**” address (32-bits, 4G)
 - 8032’s 64K address spaces are mapped into regions of the 4G physical address space
 - The E5’s mappers translate the 8032’s logical address into an E5 physical address
 - Technology-independent “**Symbolic**” address
 - Re-useable, “plug and play” approach

How to Define an Address


- **SIZE** of the address to decode
 - Ranges from a single byte to a 4G region
- Which address **SPACE** to decode
 - The 8032 has three user spaces
- The **SYMBOLIC** name for the decoded address
 - Technology independent
 - Designed for module re-use
 - Forward compatible, “plug and play”

CSI Address Selectors

- Distributed, integrated address decoders
- Up to 200 per device
- Multi-purpose
 - SELECTOR - decode read and write
 - CHIPSEL - decode read and chip select
 - DMACTRL - distributed DMA control
- “Plug and Play” versatility


Selector

Schematic

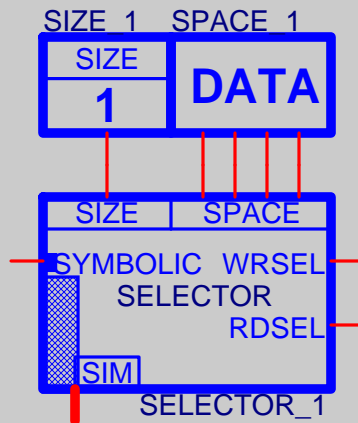

- Separately decode read and write transactions
- Use SELECTORW if you need a wait-state

Selector (Hardware)

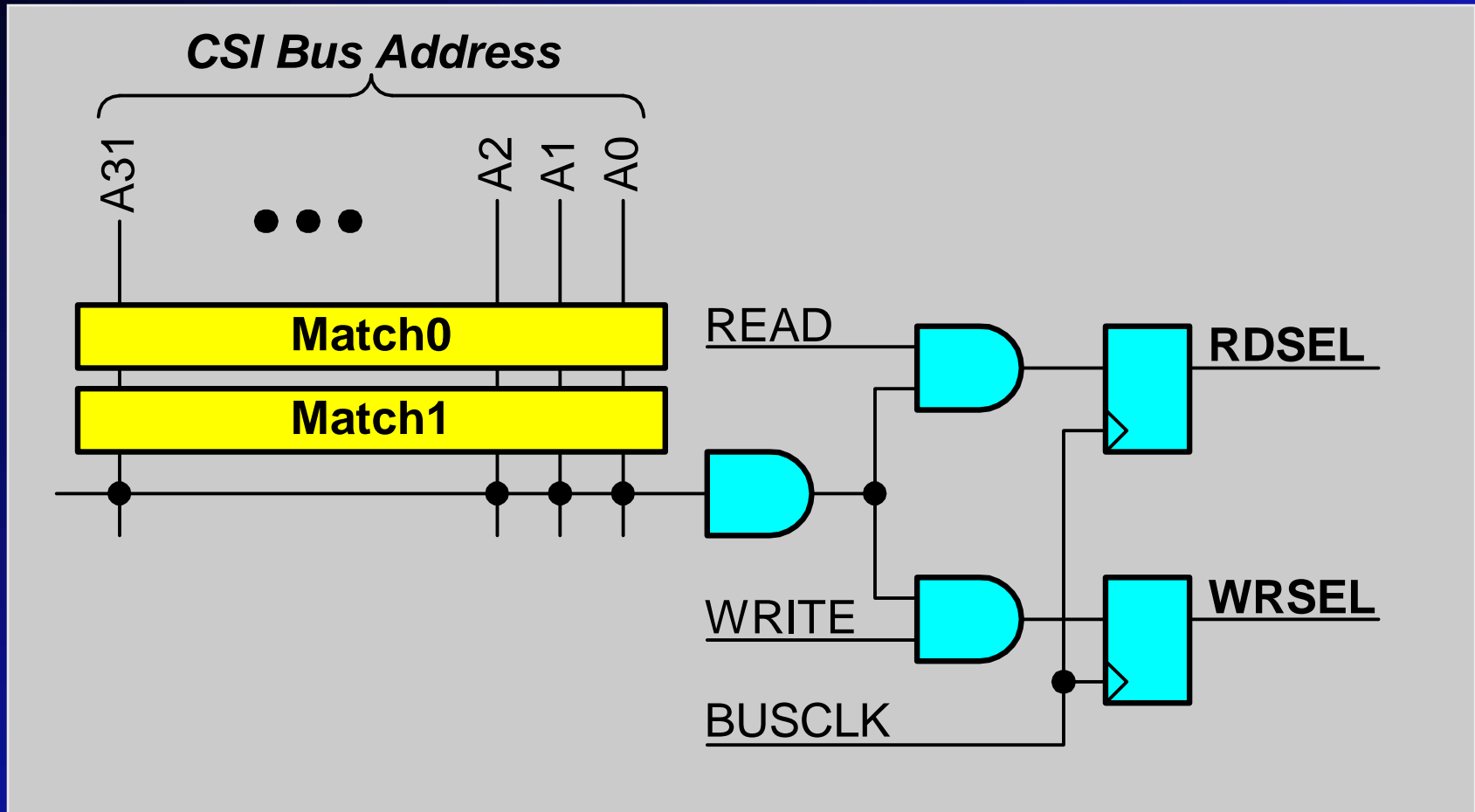

Selector Programming Example

Match1	Match0	Purpose
0	0	Disabled
0	1	An=1
1	0	An=0
1	1	Don't care

- Each address bit individually decoded
 - Match on High
 - Match on Low
 - Match on either (don't care)
- Final decode is the AND of all 32 lines

Selector (VHDL)

Instantiate

```
architecture TRISCEND of MYDESIGN is

component SELECTOR
  port (
    SYMBOLIC: in std_logic;
    SIZE      : in std_logic;
    DATA     : in std_logic;
    CODE      : in std_logic;
    SPC1      : in std_logic;
    SPC0      : in std_logic;
    WRSEL     : out std_logic;
    RDSEL     : out std_logic;
    SIM      : inout std_logic_vector(127 downto 0)
  );
end component;
```

Use

```
begin
  MYSEL : SELECTOR port map (
    SYMBOLIC => my_symbolic,
    SIZE     => my_size,
    DATA    => my_data,
    CODE     => my_code,
    SPC1     => my_spc1,
    SPC0     => my_spc0,
    WRSEL    => my_wrsel,
    RDSEL    => my_rdsel
  );
```

Ports vs. Parameters


- No easy way to define parameters in schematic editors
- Limited parameterization in VHDL and Verilog
- Parameters are notoriously difficult to simulate
- Chisel supports both ports and parameters
 - A variable beginning with a period is a **port**
 - A variable beginning with a colon is a **parameter**

Selector (Chisel)

```
module example {  
  
    parameter string my_symbolic = "MY_SYMBOLIC";  
  
    output my_wrsel;  
    output my_rdsel;  
  
    selector MYSEL (  
        .wrsel=my_wrsel,  
        .rdsel=my_rdsel,  
        :symbolic=my_symbolic,  
        :size="1",  
        :isdataspace=true  
    );  
  
}
```



Chip Select

Schematic

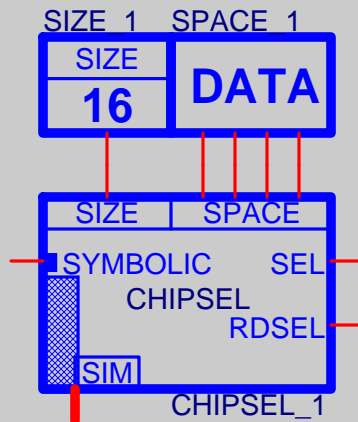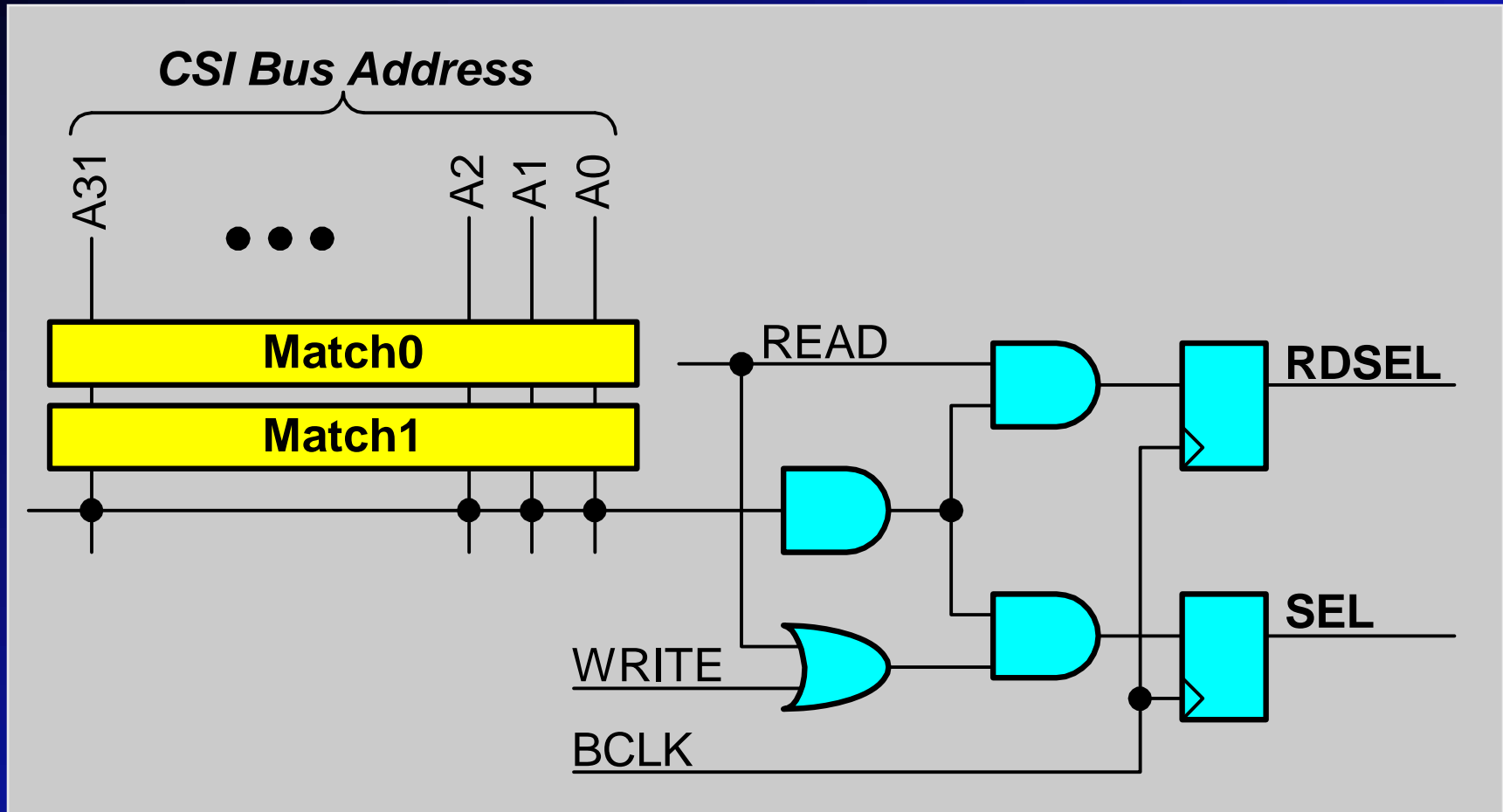

- SEL indicates any transaction to selected address space
- RDSEL asserted only on read to selected address space (indicates direction of transfer)

Chip Select (Hardware)



Chip Select (VHDL)

Instantiate

```
architecture TRISCEND of MYDESIGN is

component CHIPSEL
  port (
    SYMBOLIC: in std_logic;
    SIZE      : in std_logic;
    DATA     : in std_logic;
    CODE      : in std_logic;
    SPC1      : in std_logic;
    SPC0      : in std_logic;
    SEL       : out std_logic;
    RDSEL     : out std_logic;
    SIM      : inout std_logic_vector(127 downto 0)
  );
end component;
```

Use


```
begin
  MYSEL : CHIPSEL port map (
    SYMBOLIC => my_symbolic,
    SIZE    => my_size,
    DATA   => my_data,
    CODE    => my_code,
    SPC1    => my_spc1,
    SPC0    => my_spc0,
    SEL     => my_sel,
    RDSEL   => my_rdsel
  );
```

Chip Select (Chisel)

```
module example {  
  
    parameter string my_symbolic = "MY_SYMBOLIC";  
  
    output my_sel;  
    output my_rdsel;  
  
    chipsel MYSEL (  
        .sel=my_sel,  
        .rdsel=my_rdsel,  
        :symbolic=my_symbolic,  
        :size="16",  
        :isdataspace=true  
    );  
  
}
```

Defining the SIZE

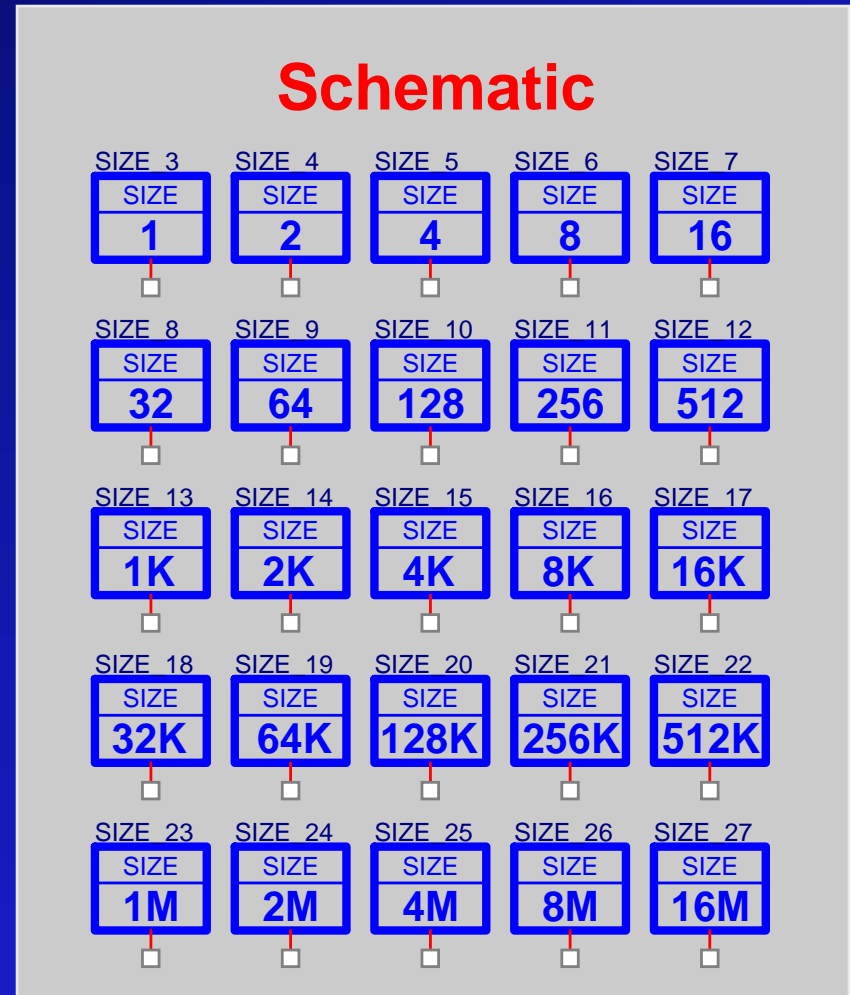- Defines number of bytes selected
 - Defines number of “don’t care” bits for low-order address lines
- Always a power of 2
 - SIZE1 = single byte
 - SIZE1K = 1 Kbyte
 - SIZE1M = 1 Mbyte
- Up to 16M in E5 family



Size (VHDL)

Instantiate

```
architecture TRISCEND of MYDESIGN is  
  component SIZEx  
    port (  
      O : out std_logic  
    );  
  end component;
```

SIZE1, SIZE1K,
SIZE1M, etc.

Use

```
begin  
  MYSIZE : SIZEx port map (  
    O => my_size  
  );
```

Size (Chisel)

- Parameter on various Selector functions
- Example: **:size="16K"**


Defining the SPACE

- Defines the address space for the decode

- Data (XDATA)
- Code
- Special Function Registers (SFRs)

- Defines the upper byte presented on the address bus

- Mappers

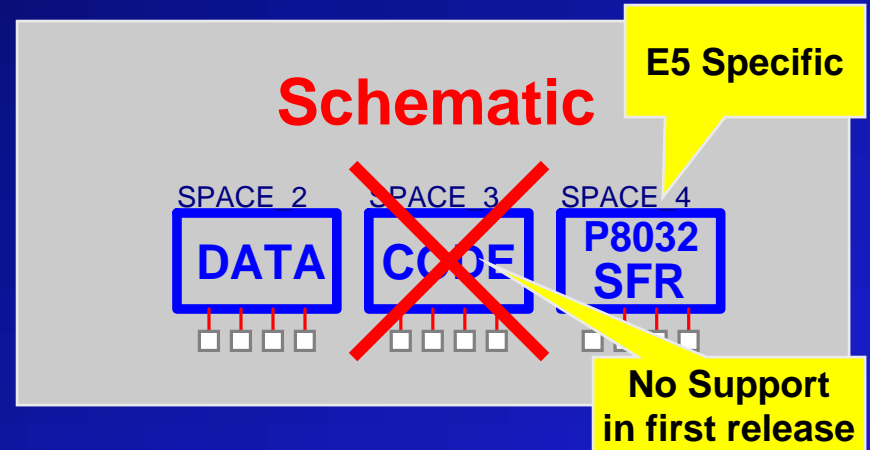

- 8032 Address Spaces

- XDATA is 64K
- CODE is 64K
- SFR is about ~90 bytes

SPACE (VHDL)

Instantiate

architecture TRISCEND of MYDESIGN is

component DATA

DATA, CODE,
SFR, etc.

port (

DATA : out std_logic;

CODE : out std_logic;

SPC1 : out std_logic;

SPC0 : out std_logic

);

end component;

Use

begin

MYSPACE : DATA port map (

DATA => my_data,

CODE => my_code,

SPC1 => my_spc1,

SPC0 => my_spc0


);

SPACE (Chisel)

- Parameter on various Selector functions
- Example: **:isdataspace=true**

SYMBOLIC

Schematic

 

- Defines a net as a symbolic name
- Symbolic inputs are treated separately from normal input nets
- Maintains simulation capability (no parameters)

SYMBOLIC (VHDL)

Instantiate

```
architecture TRISCEND of MYDESIGN is  
  
component SYMBOLIC  
  port (  
    I : in std_logic  
  );  
end component;
```


Use

```
begin  
  MYADR : SYMBOLIC port map (  
    I => my_addr  
  );
```

SYMBOLIC (Chisel)

- Parameter on various Selector functions
- Example: `:symbolic="my_addr"`

Example: Read/Write Register

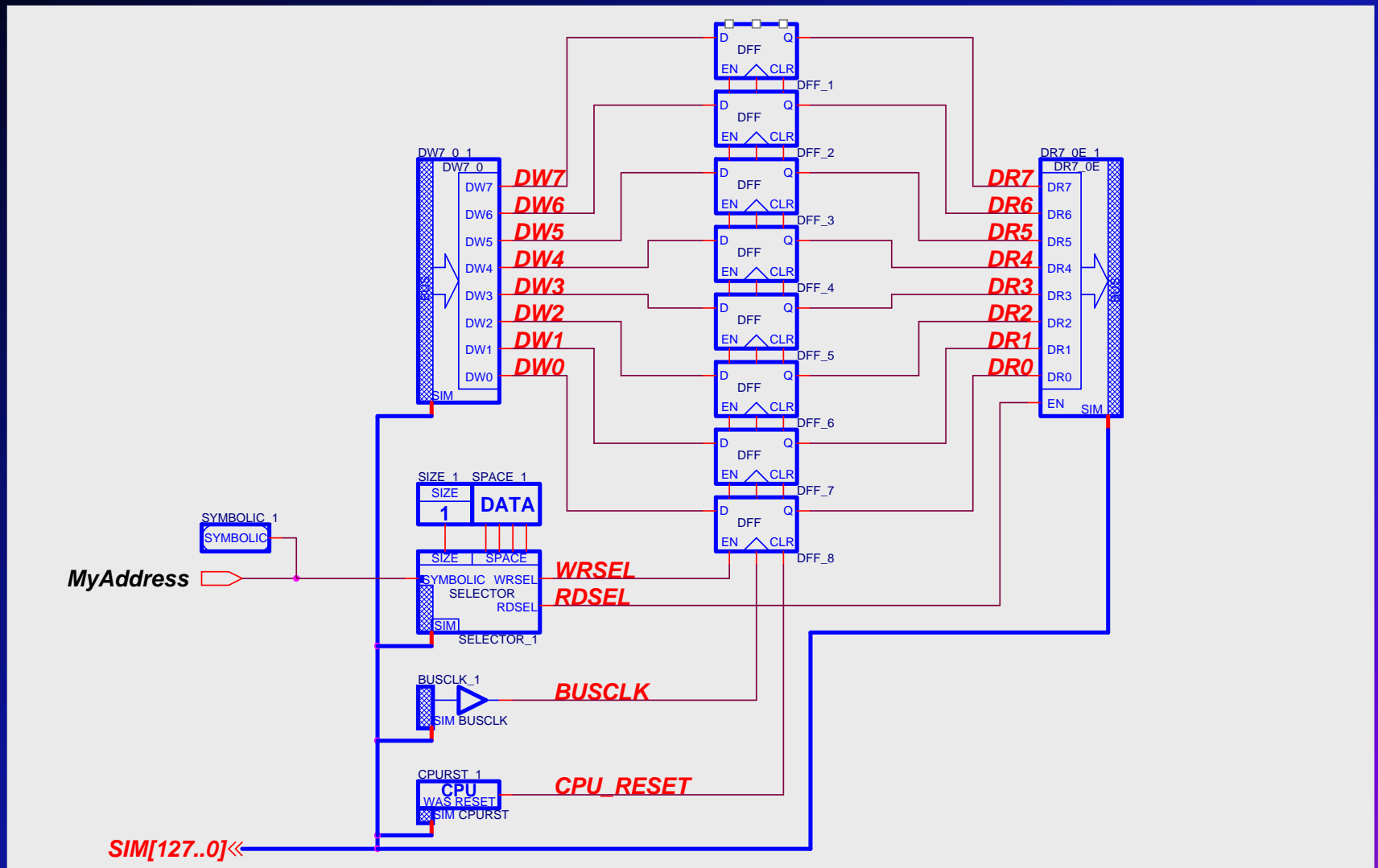

Interface to Compilers/Assemblers

- FastChip Address Allocation
 - Examines information from each Selector function
 - SIZE, SPACE, SYMBOLIC
 - Creates address assignment for each address space
- Allocation file (.al) created by FastChip
- Header file contains address information for compiler/assembler

Example Allocation File

- Located in 'data/ProjectRegistry/<proj>'
- File is named '<proj>.al'

```
// Allocation written 7/10/99 5:27 AM
// By FastChip Version Preview 4 Release 061999 Build 08
// Summary of zones:
// -----
```

Mapper programming information

```
// CRU_DATA (DMAP3) L:0xff00:0xffff P:0x2_0e00:0x2_0eff F:0 T:0x98 A:0x0
// USER_DATA_C (DMAP2) L:0x0000:0x1fff P:0x1_8000:0x1_9fff F:0 T:0x90 A:0x0
// USER_DATA_D (DMAP1) L:0x0000:0xffff P:0x10_0000:0x10_ffff F:1 T:0x88 A:0x0
// SRAM_DATA (DMAP0) L:0x0000:0xffff P:0x2_0000:0x2_ffff F:0 T:0x80 A:0x0
// USER_CODE_B (CMAP1) L:0x0000:0x7fff P:0x1_0000:0x1_7fff F:0 T:0x28 A:0x48
// ROM_CODE (CMAP0) L:0x0000:0x03ff P:0x0000:0x03ff F:0 T:0x20 A:0x40
// SFR_DATA (XMAP) L:0x0080:0x00ff P:0x1f_ff80:0x1f_ffff F:1 T:0xc0 A:0xe0
```

S E520JTAG;

```
A "Result.CMDREG" "Result" "USER_DATA_D" 0x2000; // 0x10_2000
"Switch.STATREG" "Switch" "SFR_DATA" 0x009a; // 0x1f_ff9a
```

Allocation style

Assigned user locations

Generated Header File




- Header file created during Generate
- Saved in either A51 (.inc) or C51 (.h) format, targeted to Keil
- Contains compiler/assembler view of allocation (plus much more)

```
//===== BEGIN SOFT MODULE REGISTER DECLARATIONS =====  
  
//----- Module Result  
  CHAR_XDATA (Result,0x2000)  
  
//----- Module Switch  
  sfr Switch = 0x9a;  
  
//===== END SOFT MODULE REGISTER DECLARATIONS =====
```

Converting an Existing 8032 Design to CSI Bus

Data Interface


Original Design

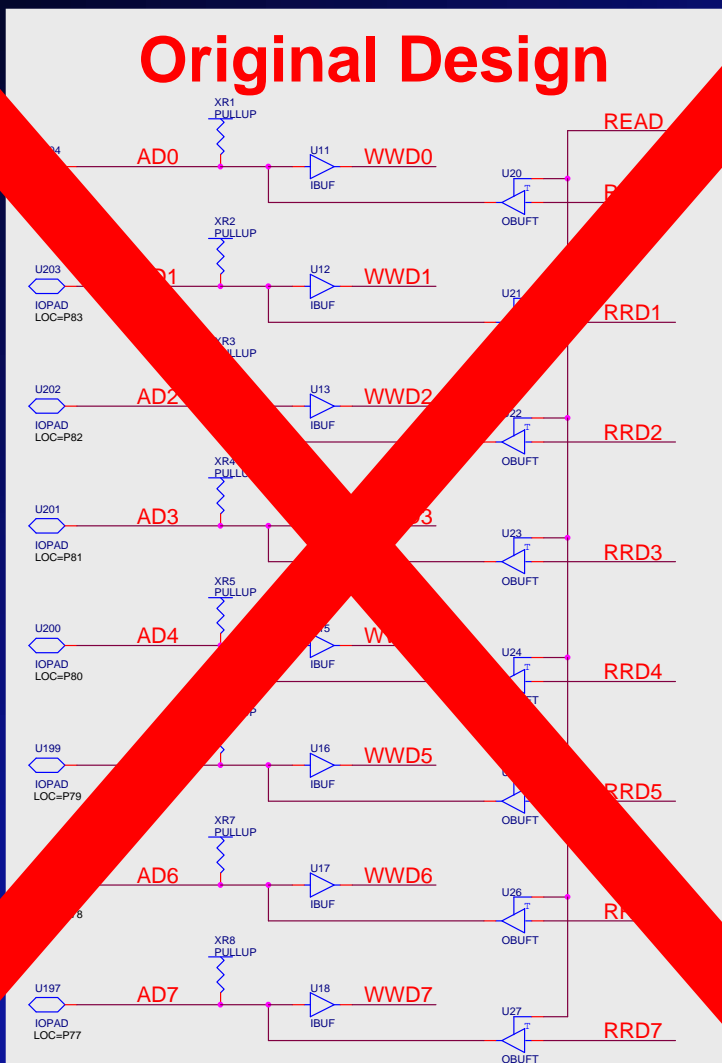

- 8032 data interface embedded on CSI bus
- Saves I/O pin count
- Reduces power consumption and EMI
- Replaced by CSI Bus Data Write and Data Read primitives


Address Decoding

Original Design

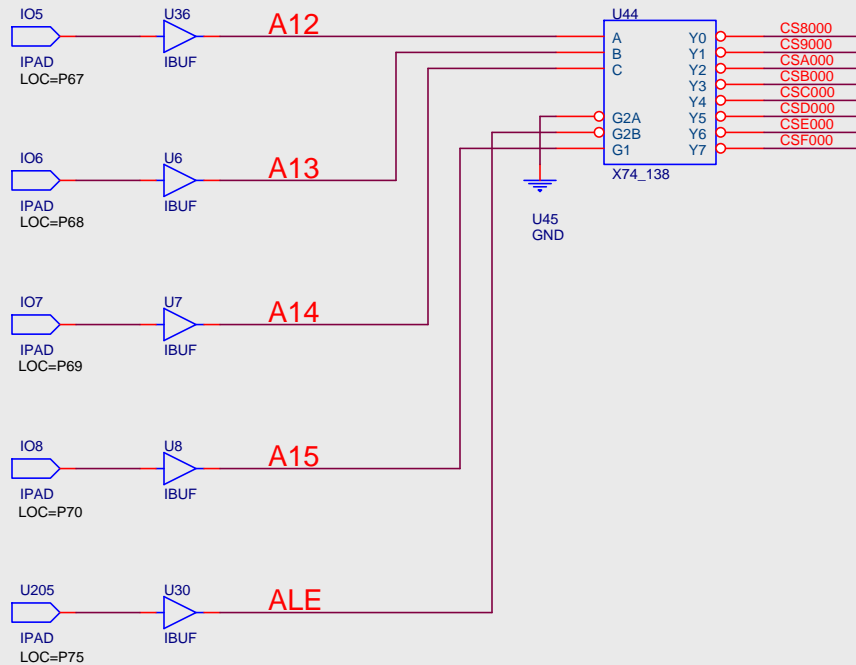

- Original 8032 had multiplexed address/data (ALE)
- Expensive to decode full address bus
- Address lines embedded on CSI bus
- Saves I/O pin count
- Reduced power, EMI

Addressing Registers

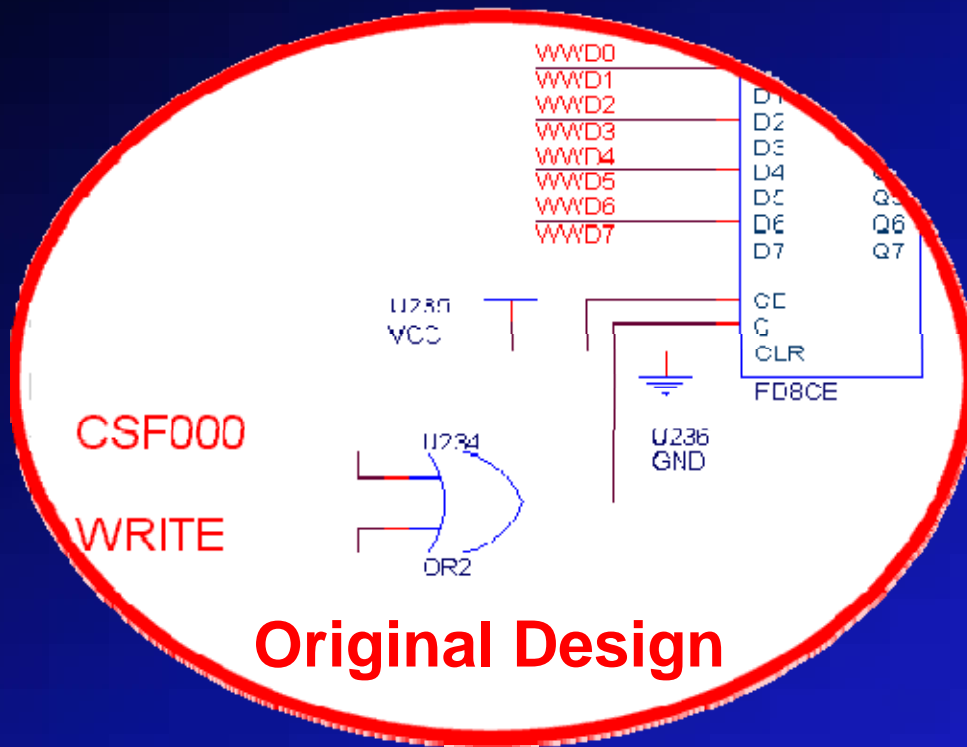

- CSI bus Selectors replace address decoding logic in the application
- See Read/Write Example
- CSI approach is safe, synchronous design

Address Decoding (VHDL)

```
CE_ADDR <= TRUE when ((ADDR = "10000000") or  
                      (ADDR = "10000001") or  
                      (ADDR = "10000010") or  
                      (ADDR = "10000011") or  
                      (ADDR = "10000100") or  
                      (ADDR = "10000101") or  
                      (ADDR = "10000110") or  
                      (ADDR = "10000111") or  
                      (ADDR = "10001000") or  
                      (ADDR = "10001001") or  
                      (ADDR = "10001010") or  
                      (ADDR = "10001011") or  
                      (ADDR = "10001100") or  
                      (ADDR = "10001101") or  
                      (ADDR = "10001110") or  
                      (ADDR = "10001111"))
```

Decodes
16 bytes

Specifying
logical address,
not portable


Final chip select
signal is
active-Low

8032 signal
indicating
address cycle

```
else FALSE;
```

```
CE <= '0' when ((CE_ADDR) and (ALE = '0')) else '1';
```

CSI Bus Equivalent

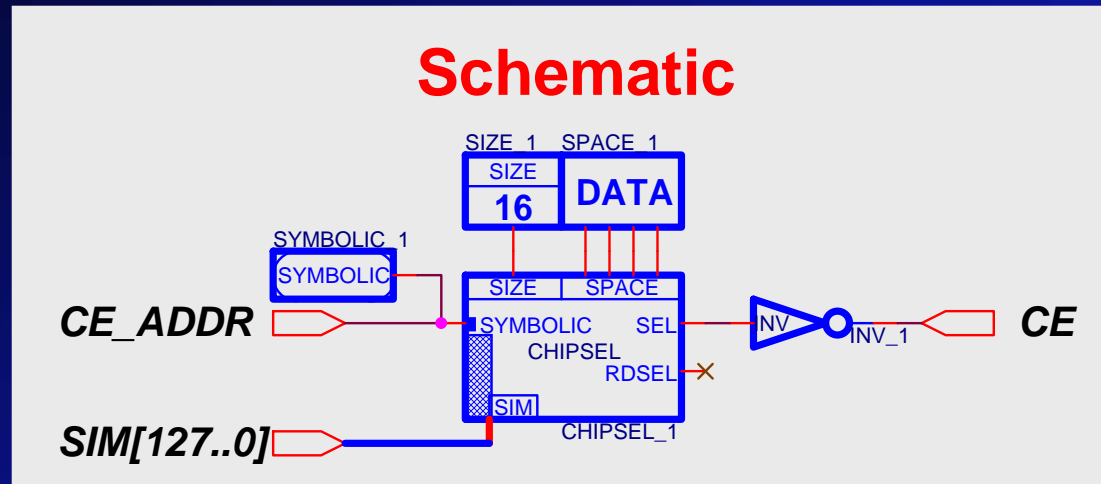

- Function is a chip select (decode independent of Read or Write)
- For existing applications, most peripherals are in DATA space


Creating Address Structures

Relative Assignments and Offsets

Creating Memory Structures

- Symbolic addressing allows technology-independent design
- How do you create a memory structure?
 - Very important for DMA operations
 - DMA requires contiguous addresses
- Need ability to specify relationships
 - Parent-child relationships
 - Offset between addresses

Relative Addressing Example

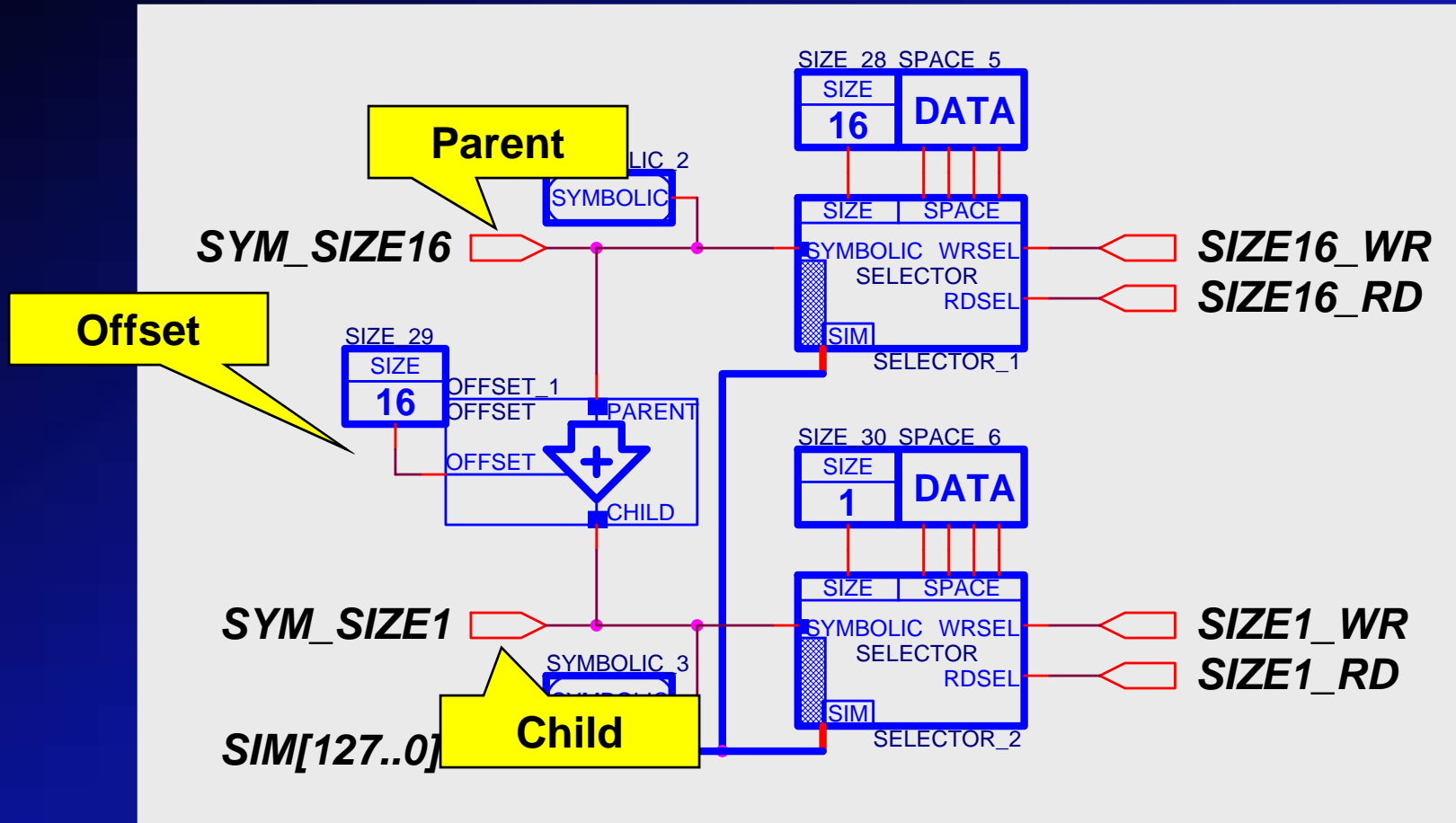

OFFSET (VHDL)

Instantiate

architecture TRISCEND of MYDESIGN is

component OFFSET

port (

CHILD : in std_logic;

PARENT : in std_logic;

OFFSET : in std_logic

);

end component;

Use

begin

MYOFFSET : OFFSET port map (

CHILD => my_child,

PARENT => my_parent,

OFFSET => my_offset

);

OFFSET (Chisel)

Parent

```
selector MYSIZE16 (  
  .wrsel=size16_wr,  
  .rdsel=size16_rd,  
  :symbolic="SYM_SIZE16",  
  :size="16",  
  :isdataspace=true  
);
```

Child

```
selector MYSIZE1 (  
  .wrsel=size1_wr,  
  .rdsel=size1_rd,  
  :symbolic="SYM_SIZE1",  
  :size="1",  
  :isdataspace=true,  
  :relative="SYM_SIZE16",  
  :offset=16  
);
```

Offset

Relative Addressing Rules

- Child must be aligned to a power-of-2 of its size
 - Byte aligned for SIZE1
 - Aligned to 1K boundary for SIZE1K
- Parent and child must be in same address space (no mixing)


DMA Operations

DMA Control Registers

- Selectors alter ego: The DMA Control Register
- Provides distributed DMA services to functions within the CSL logic
- DMA controller provides “proxy” bus mastering services for CSL peripherals
- DMA Control Registers work in conjunction with DMA controller


DMA Control Register

Schematic

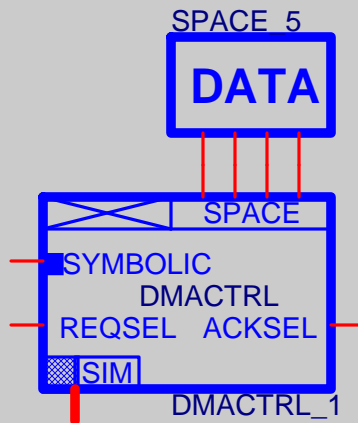


- Provides Request and Acknowledge steering to selected DMA channel
- Always one byte
- Exists in either Data or SFR space
- Control register located at SYMBOLIC address


DMA Control Register (Physical Model)

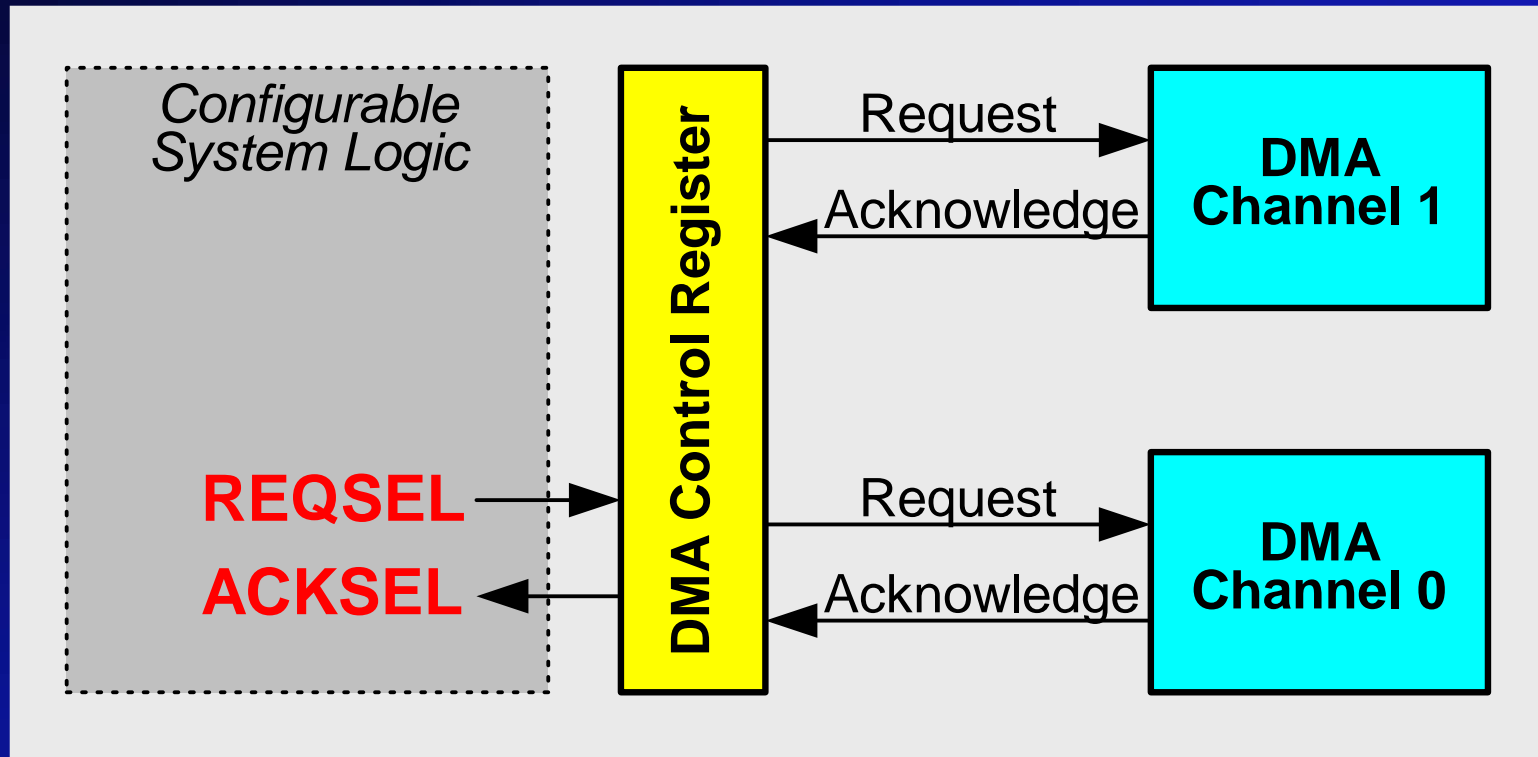


Request Steering (REQSEL)

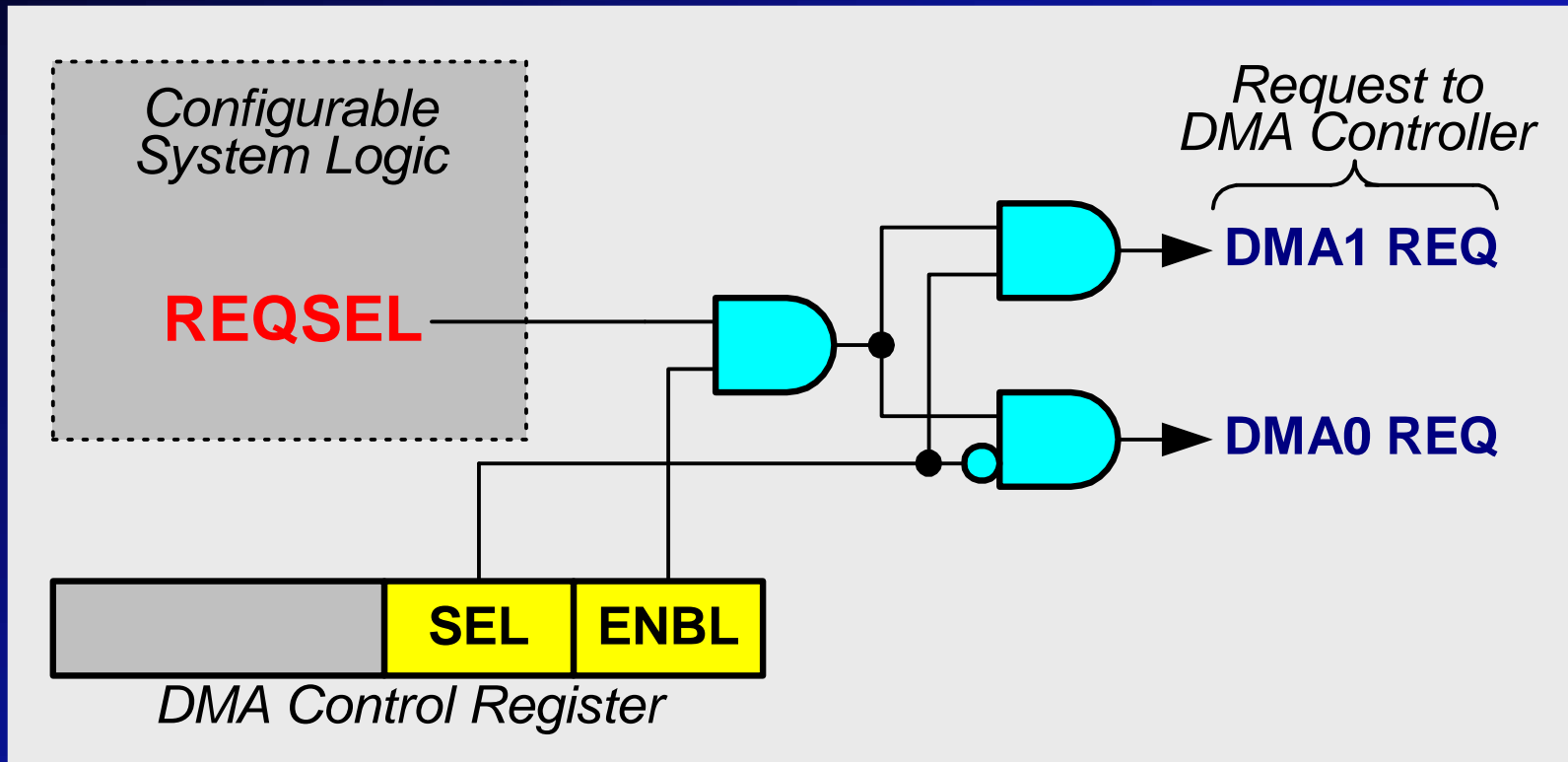

Acknowledge Steering (ACKSEL)

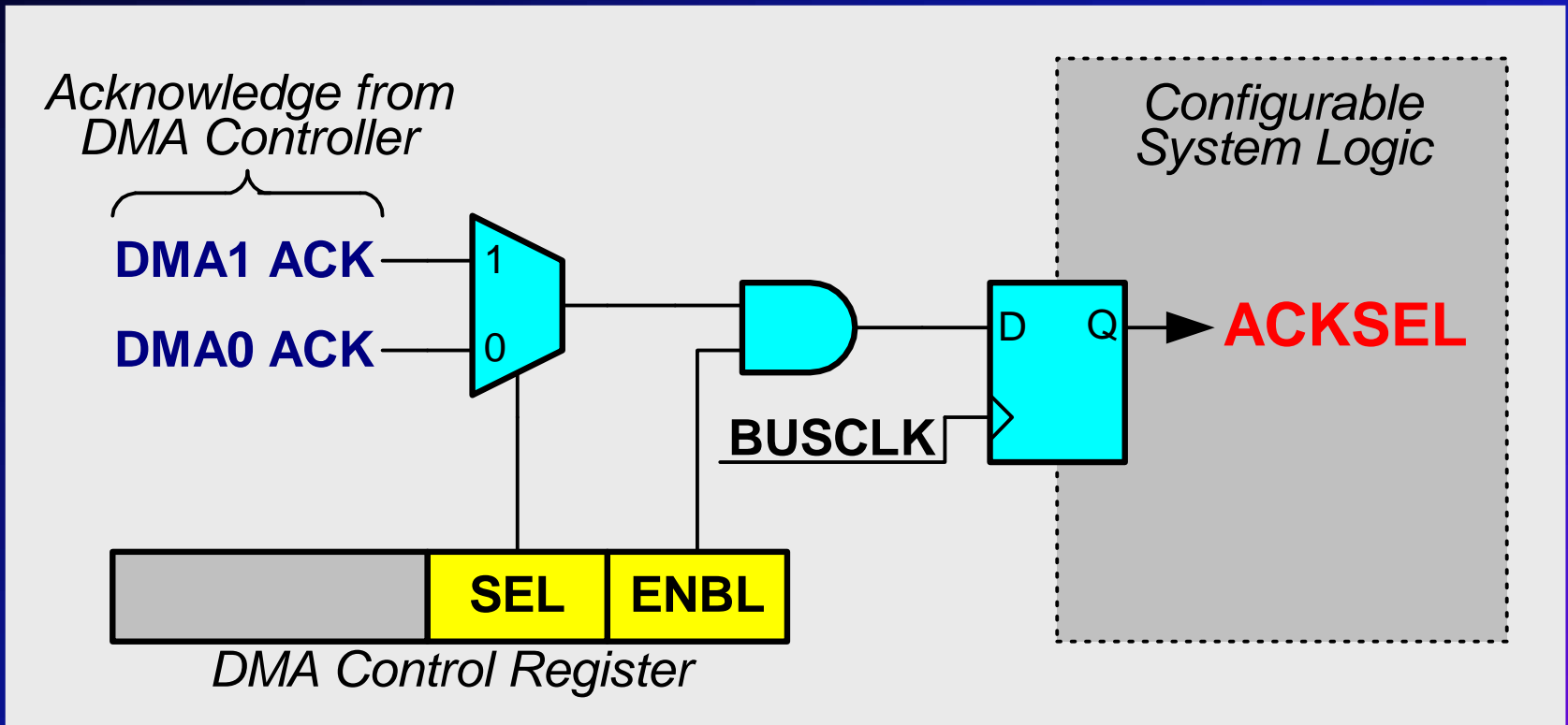

DMA Control Register Details

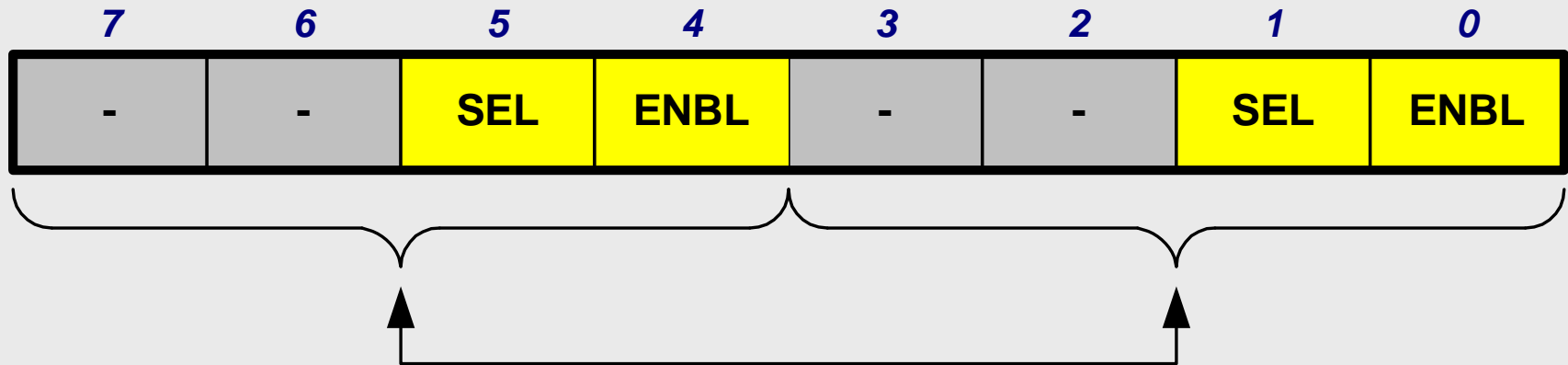

Write both nibbles with duplicate data.

Read register and OR bits from each nibble.

- Due to data distribution to Selectors, watch out for these details!

DMA Control Register (VHDL)

Instantiate

```
architecture TRISCEND of MYDESIGN is

component DMACTRL
  port (
    SYMBOLIC : in std_logic;
    DATA     : in std_logic;
    CODE      : in std_logic;
    SPC1      : in std_logic;
    SPC0      : in std_logic;
    REQSEL    : in std_logic;
    ACKSEL    : out std_logic;
    SIM      : inout std_logic_vector(127 downto 0)
  );
end component;
```


Use

```
begin
  MYSEL : DMACTRL port map (
    SYMBOLIC => my_symbolic,
    DATA    => my_data,
    CODE     => my_code,
    SPC1     => my_spc1,
    SPC0     => my_spc0,
    REQSEL   => my_reqsel,
    ACKSEL   => my_acksel
  );
```


DMA Control Register (Chisel)

```
module example {  
  
    parameter string my_symbolic = "MY_SYMBOLIC";  
  
    input my_reqsel;  
    output my_acksel;  
  
    dmactrl MYSEL (  
        .reqsel=my_reqsel,  
        .acksel=my_acksel,  
        :symbolic=my_symbolic,  
        :isdataspace=true,  
        :enabled=false,  
        :channel=0  
    );  
  
}
```


DMA Write Example

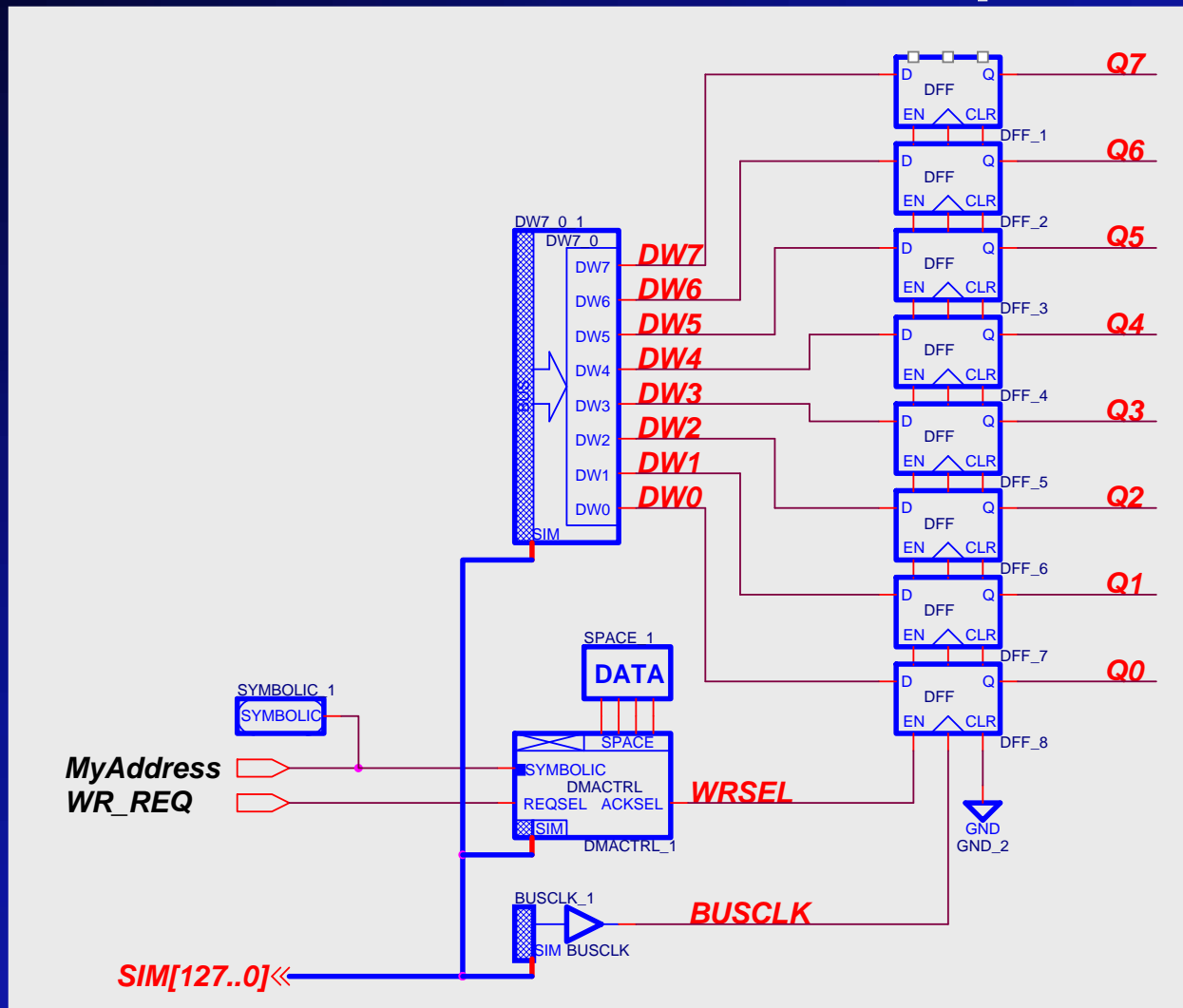


DMA Write Simulation

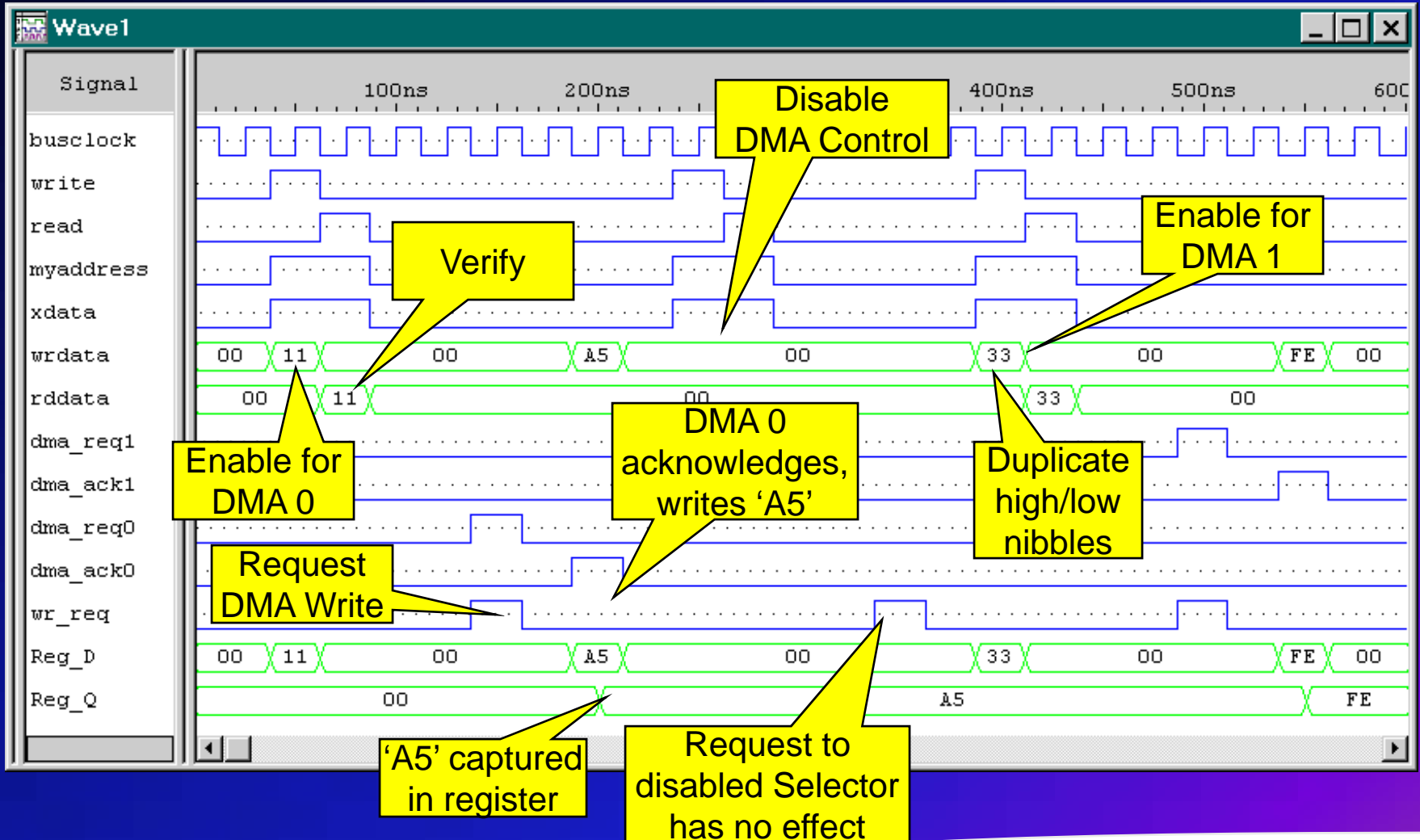

DMA Read Example

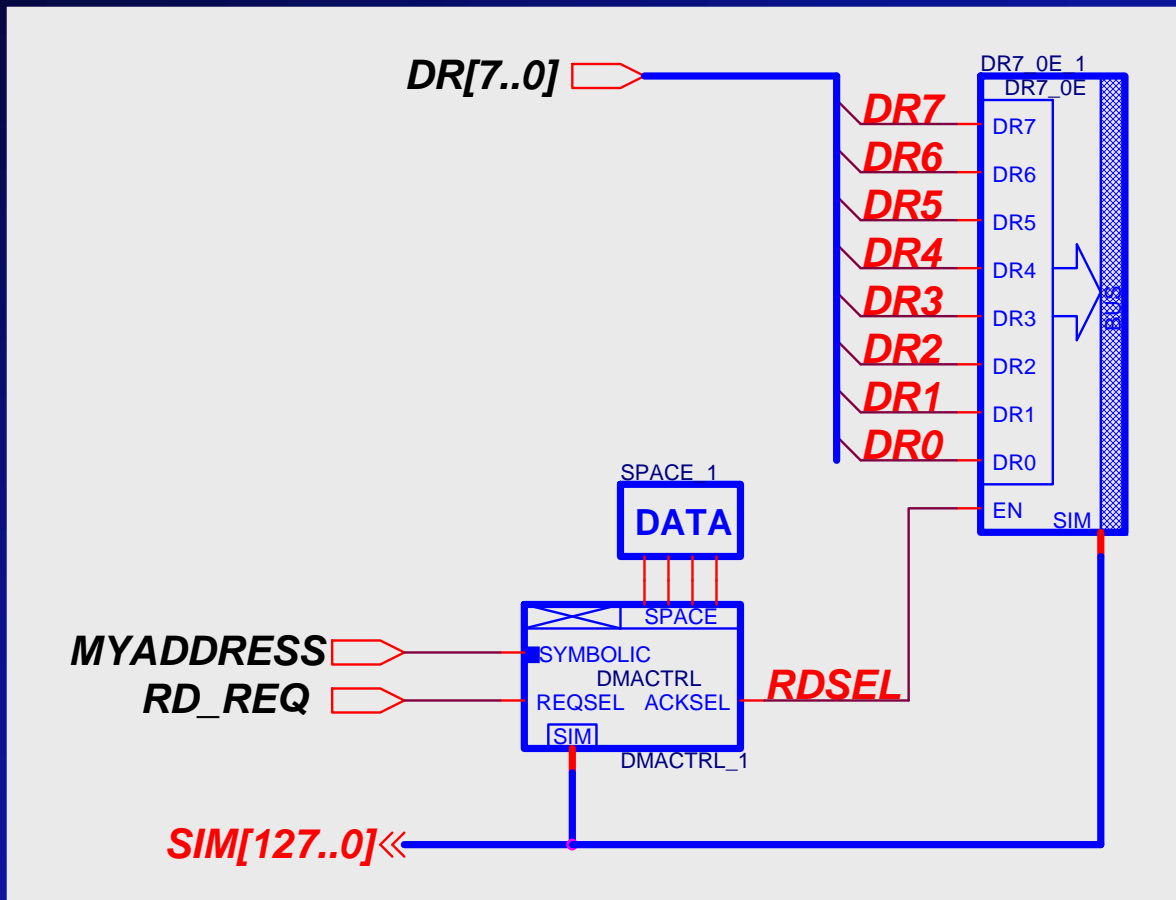

DMA Read Simulation

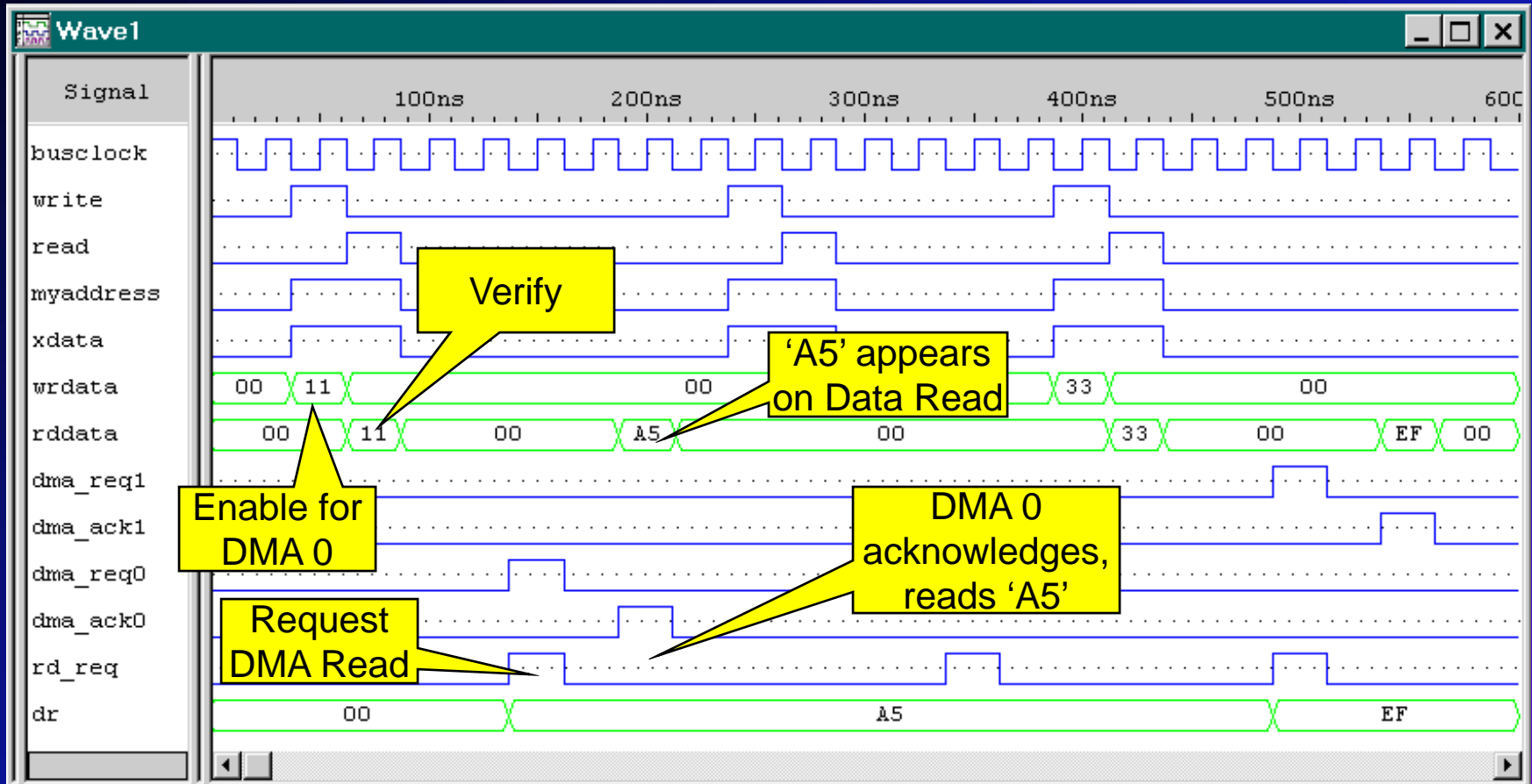

CSI SIM Bus Models


The CSI Bus Simulation Model

- What's that 128-bit bus connected to my bus symbols?
 - 128-bit bidirectional bus
 - Contains all CSI bus signals, forward compatible with 32-bit architectures
 - Simplifies simulation for CSI bus peripherals
 - Easy connection to CSI bus primitives
- E5_CSI top-level symbol drives SIM bus


CSI SIM Bus Signals

CSI Bus Signal	Simulation Bus Signal
Data Write[31:0]	SIM[31:0]
Data Read[31:0]	SIM[63:32], Wired-OR
Address[31:0]	SIM[95:64]
Bus Clock	SIM[96]
Read	SIM[97]
Write	SIM[98]
Wait	SIM[99], Wired-OR
Reserved	SIM[100]
Breakpoint	SIM[101], Wired-OR
Reserved	SIM[102]
DMAREQ[7:0]	SIM[109:103], Wired-OR
DMAACK[7:0]	SIM[117:110]
DATA access	SIM[118] (8032 – XDATA)
CODE access	SIM[119]
SPC1 access	SIM[120] (8032 – SFR latch)
SPC2 access	SIM[121] (8032 – SFR pin)
Reserved	SIM[127:122]


E5_CSI Simulation Driver

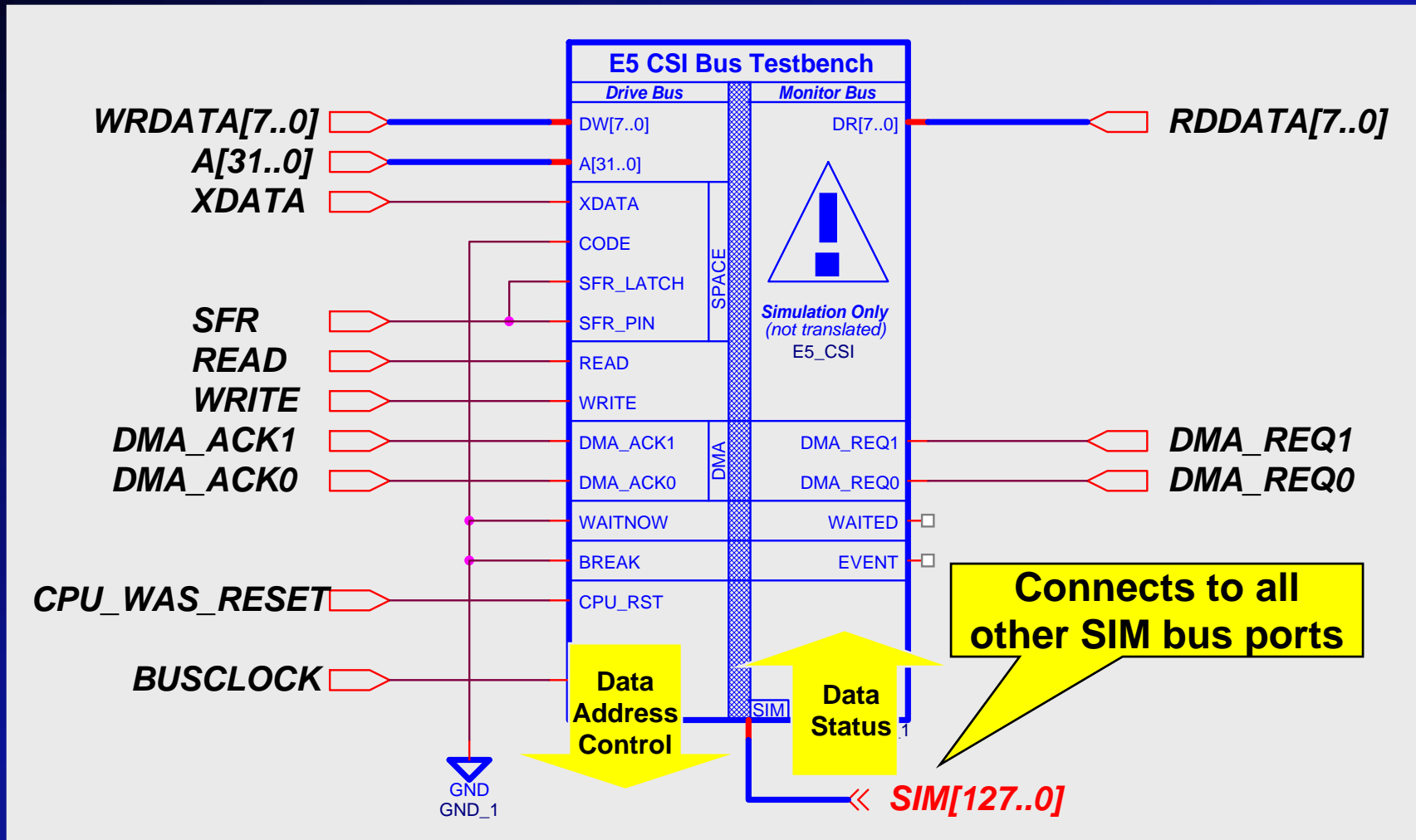

Example: Read/Write Register

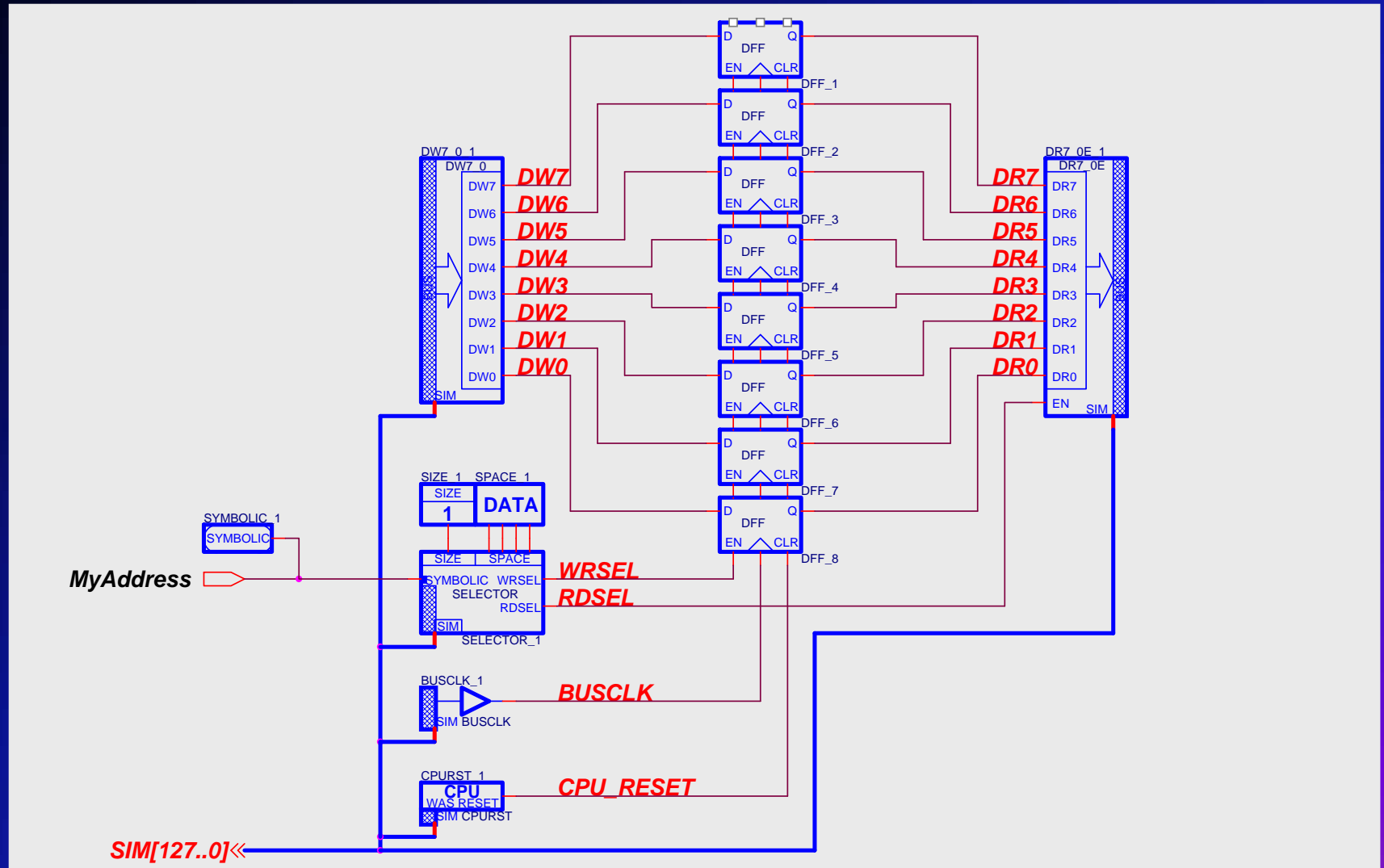


CSI Bus Simulation Example

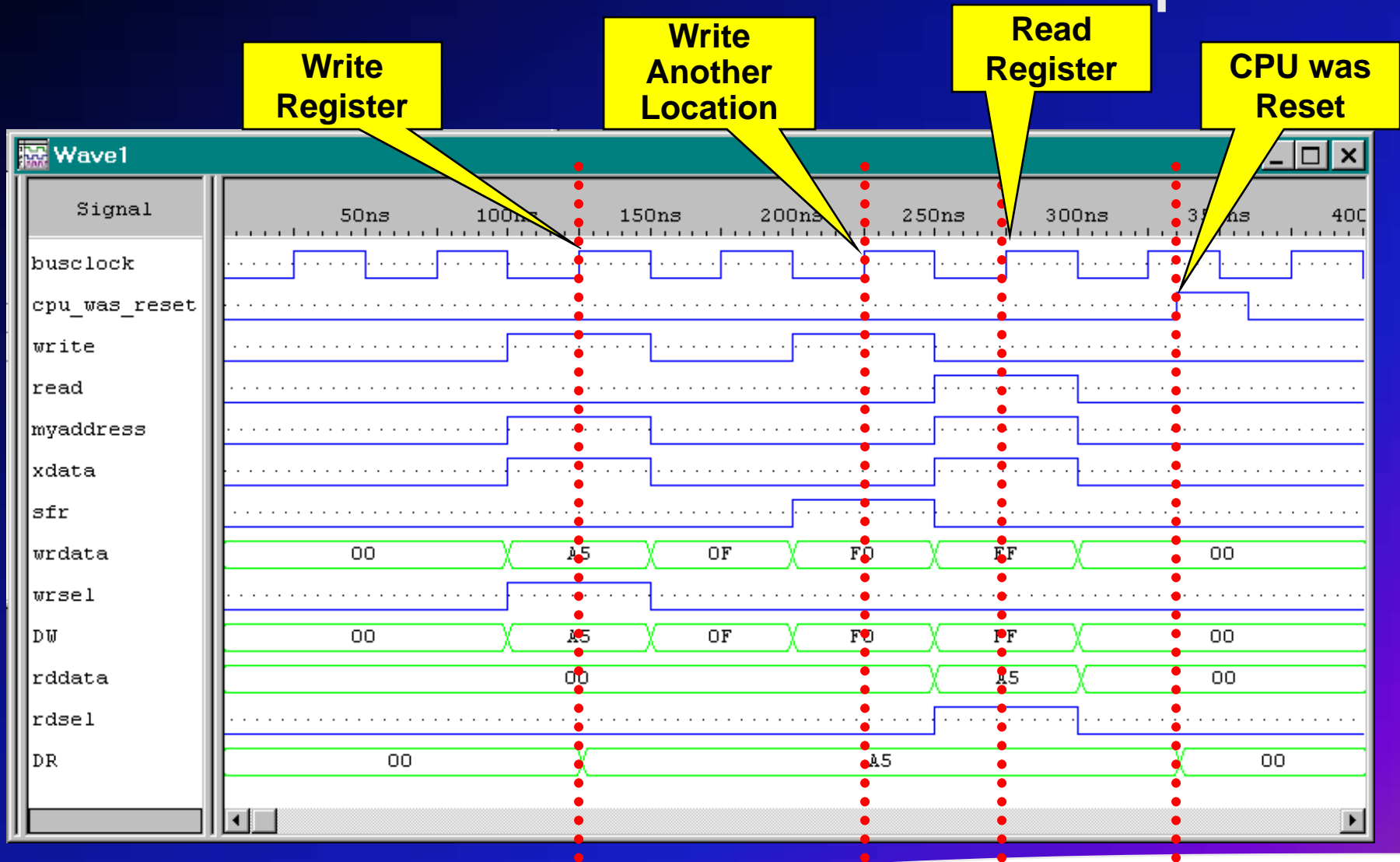

Wait-State and Breakpoint

Wait-State Control

Schematic

 


- WAITNEXT holds the next bus cycle
- WAITED indicates that a wait-state happened during the last bus cycle

Wait-State Rules


- The CSI Bus Supports Wait-States, but with a few restrictions
- If a peripheral asserts a wait-state, the first wait-state is asserted by the associated Selector
 - SELECTORW
 - CHIPSELW
 - There are no wait-states on DMA transfers

Wait-State Examples


Zero Wait-States

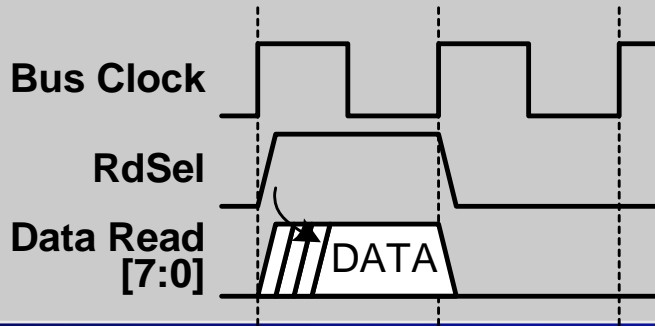

One Wait-State

 

Multiple Wait-States

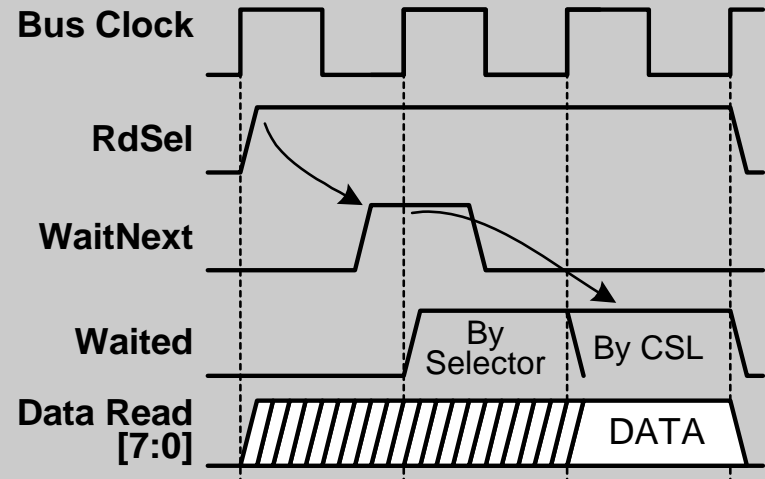

Wait-State Control (VHDL)

Instantiate

```
architecture TRISCEND of MYDESIGN is  
  
  component WAITCTRL  
    port (  
      WAITNEXT : in    std_logic;  
      WAITED    : out  std_logic;  
      SIM       : inout std_logic_vector(127 downto 0)  
    );  
  end component;
```

Use

```
begin  
  MYWAIT : WAITCTRL port map (  
    WAITNEXT => my_waitnext,  
    WAITED   => my_waited  
  );
```


Wait-State Control (Chisel)

```
module example {  
  
    input my_waitnext;  
    output my_waited;  
  
    waitnext (.i=my_waitnext);  
    waited (.o=my_waited);  
  
}
```


Example Wait-State Design

- Peripheral supports single-cycle reads but requires a three-cycle write
- CSI wait-state mechanism requires at least one wait-state if you have any wait-states

Example Wait-State Schematic

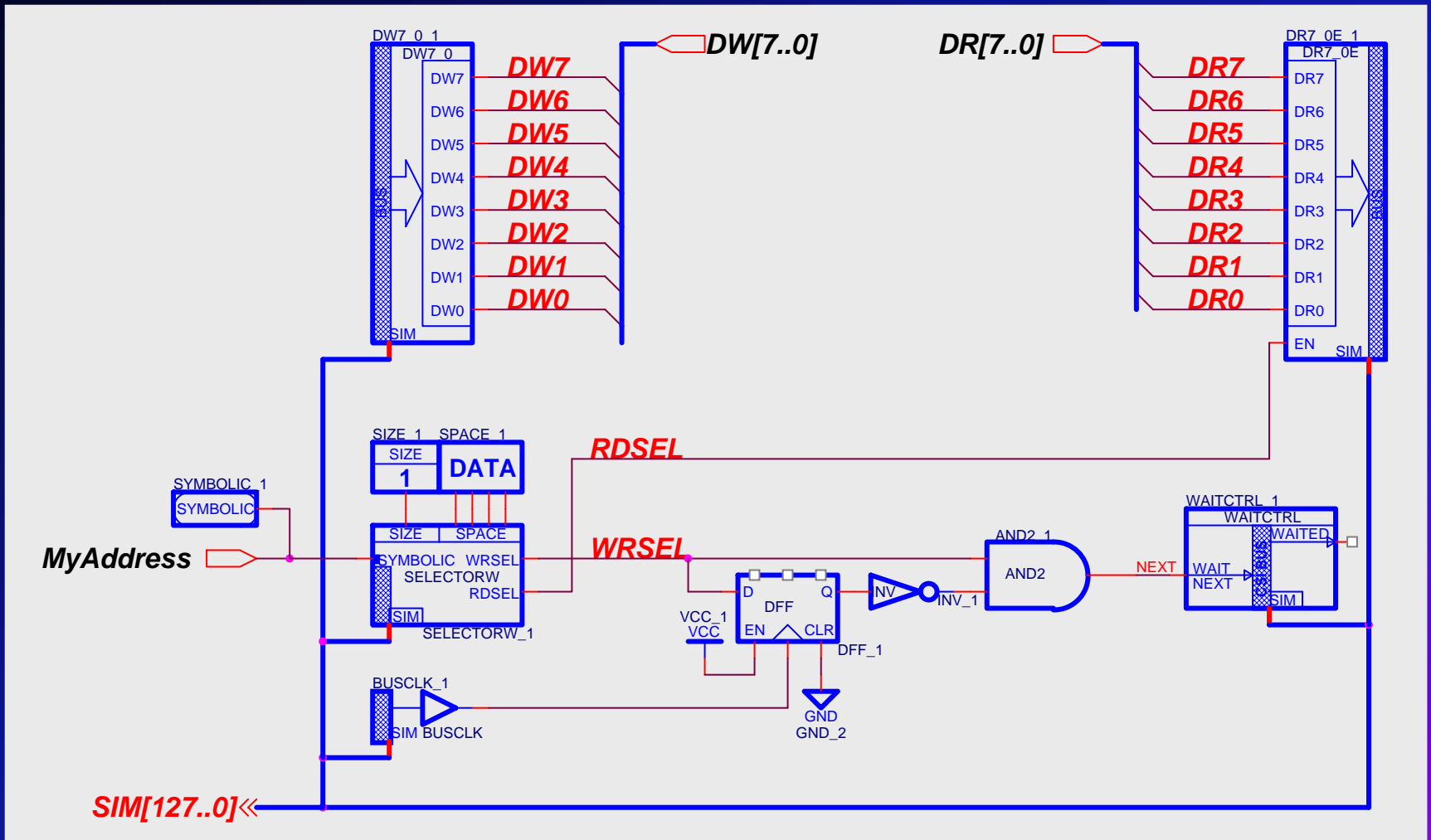

Example Wait-State Simulation

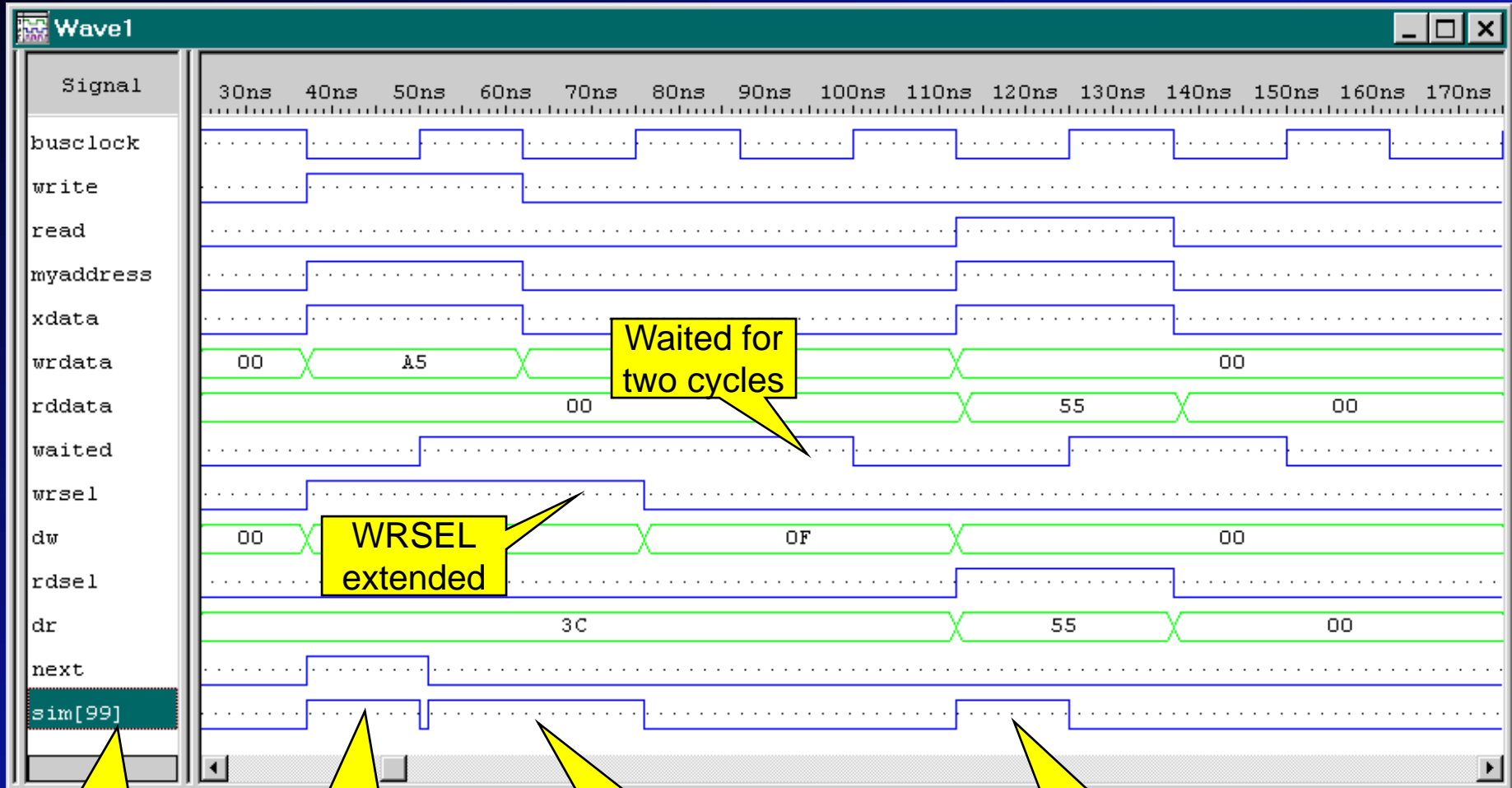

Wait signal on SIM bus


Wait-state from Selector

Wait-state from logic

Wait-state from Selector

Hardware Breakpoint

Schematic

 

- BREAK causes a hardware breakpoint
- EVENT indicates that a hardware breakpoint is happening

Hardware Breakpoint (VHDL)

Instantiate

```
architecture TRISCEND of MYDESIGN is  
  
  component BRKPNT  
    port (  
      BREAK : in  std_logic;  
      EVENT  : out std_logic;  
      SIM    : inout std_logic_vector(127 downto 0)  
    );  
  end component;
```

Use

```
begin  
  MYBRK : BRKPNT port map (  
    BREAK => my_break,  
    EVENT  => my_event  
  );
```


Hardware Breakpoint (Chisel)

```
module example {  
  
    input my_break;  
    output my_event;  
  
    bpctl BREAK (.i=my_break);  
    bpevt EVENT (.o=my_event);  
}
```

Summary

- The Configurable System Interconnect bus provides easy access to “soft” peripherals
 - Data, Address, Control
 - Address Decoding
 - Simple, synchronous protocol

Questions?
Comments?
Feedback?